



## EXERCISE-1 PART - I

### Section (A)

**A-1.**  $Q_1 = 30\mu\text{C}$ ,  $C_1 = 5\mu\text{F}$

(i)  $V_1 = \frac{Q_1}{C_1} = \frac{30}{5} = 6\text{V}$  **Ans.**

(ii)  $U = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{(30 \times 10^{-6})^2}{(5 \times 10^{-6})} = 90 \mu\text{J}$  **Ans.**

(iii)  $Q_2 = 50\mu\text{C}$ ,  $C_2 = 10 \mu\text{F}$ ,  $V_2 = \frac{Q_2}{C_2} = \frac{50}{10} = 5\text{V}$ .

(a) Common potential  $V = \frac{Q_1 + Q_2}{C_1 + C_2} = \frac{30 + 50}{5 + 10} = \frac{16}{3} \text{V}$  **Ans.**

(b)  $\Delta H = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2 = \frac{1}{2} \frac{5 \times 10}{5 + 10} (6 - 5)^2 = \frac{5}{3} \mu\text{J}$  **Ans.**

(c)  $\frac{Q_1'}{Q_2'} = \frac{C_1}{C_2} = \frac{5}{10} = \frac{1}{2}$  **Ans.**

(d)  $Q_1' = C_1 V = 5 \times \frac{16}{3} = \frac{80}{3} \mu\text{C}$      $Q_2' = C_2 V = 10 \times \frac{16}{3} = \frac{160}{3} \mu\text{C}$ .

**A-2.**  $F_{\text{attraction}} = \frac{q^2}{2\epsilon_0 A}$  ;  $F_{\text{repulsion}} = kx$

$$|F_{\text{attraction}}| = |F_{\text{repulsion}}| \Rightarrow \frac{q^2}{2\epsilon_0 A} = kx$$

$$x = \frac{q^2}{2k\epsilon_0 A}$$

**A-3.**  $W = q\Delta V$   
 $W_{\text{by field}} = q(V_i - V_f) = Q(V_1 - V_2)$

**A-4.** The electric force between the plates will be balanced by the additional weight

hence  $mg = \frac{Q^2}{2A\epsilon_0} = \frac{C^2 V^2}{2A\epsilon_0}$

$$mg = \frac{\epsilon_0 AV^2}{2d^2}$$

$$m = \frac{\epsilon_0 AV^2}{2d^2 g} = \frac{\epsilon_0 \times 100 \times 10^{-4} (5000)^2}{2 (5 \times 10^{-3})^2 \times 10}$$

$m = 4.425 \text{ g}$  **Ans.**

**A-5.** Work done = change in potential energy

(i)  $W = U_f - U_i = \frac{q^2}{2C_f} - \frac{q^2}{2C_i} = \frac{q^2}{2} \left\{ \frac{x_2}{S\epsilon_0} - \frac{x_1}{S\epsilon_0} \right\} = \frac{q^2}{2} \frac{(x_2 - x_1)}{S\epsilon_0}$


(ii)  $W_{\text{ex}} + W_B = U_f - U_i = \left\{ \frac{S\epsilon_0}{x_2} - \frac{S\epsilon_0}{x_1} \right\} = \frac{\epsilon_0 SV^2}{2} \left\{ \frac{1}{x_2} - \frac{1}{x_1} \right\}$

$$W_{\text{ex}} = (U_f - U_i) - W_B = \frac{\Delta CV^2}{2} - \Delta CV^2 = -\frac{\Delta CV^2}{2} = (-) \frac{\epsilon_0 SV^2 \left( \frac{1}{x_2} - \frac{1}{x_1} \right)}{2}$$



**Section (B)**

**B-1.**

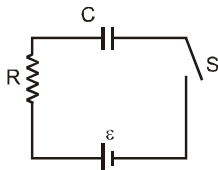

at  $t = 0$ , C is replaced by wire.

(a)  $V_{\text{max}} = \varepsilon$

(b)  $i = \varepsilon/R$

at  $t \rightarrow \infty$ , C is replaced by broken wire and now current in circuit = 0, so


(c)  $V_C = \varepsilon$

(d)  $U_C = \frac{1}{2} C\varepsilon^2$

(e)  $P_{\text{battery}} = iV = \frac{\varepsilon}{R} \varepsilon = \frac{\varepsilon^2}{R}$

(f)  $\Delta H = \frac{\varepsilon^2}{R}$


**B-2.**

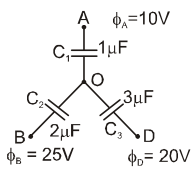

$$(V_A - V_0)C_1 + (V_B - V_0)C_2 + (V_D - V_0)C_3 = 0$$

$$V_0 = \frac{V_A C_1 + V_B C_2 + V_D C_3}{C_1 + C_2 + C_3} = \frac{10 \times 1 + 25 \times 2 + 20 \times 3}{1 + 2 + 3} = 20 \text{ V Ans.}$$

**B-3.**

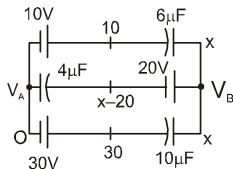

Assume माना ( $V_A = 0$ ), ( $V_B = x$ )


From conservation of charge on plates of capacitor

$$4(x - 20) + (x - 10)6 + (x - 30)10 = 0$$

$$x = 22$$

$$V_A - V_B = 0 - 22 = -22 \text{ V.}$$

**B-4.**

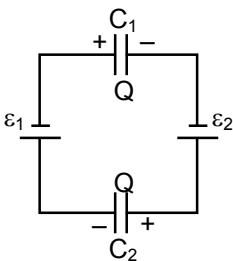

$$Q = (\varepsilon_2 - \varepsilon_1) \frac{C_1 C_2}{C_1 + C_2};$$




$$V_1 = \frac{Q}{C_1} = \frac{\epsilon_2 - \epsilon_1}{1 + \frac{C_1}{C_2}}$$

$$V_2 = -\frac{Q}{C_2} = \frac{\epsilon_1 - \epsilon_2}{1 + \frac{C_2}{C_1}}$$

**Section (C)**

**C-1.**

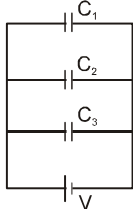

$$Q_1 = C_1 V = 1 \times 20 = 20 \mu\text{C}$$

$$Q_2 = C_2 V = 2 \times 20 = 40 \mu\text{C}$$

$$Q_3 = C_3 V = 3 \times 20 = 60 \mu\text{C}$$

$$Q_t = 120 \mu\text{C}$$

$$W_{\text{battery}} = Q_t V = 120 \times 20 = 2400 \mu\text{J}$$

$$U_C = \frac{1}{2} C_1 V^2 + \frac{1}{2} C_2 V^2 + \frac{1}{2} C_3 V^2 = \frac{1}{2} (C_1 + C_2 + C_3) V^2$$

$$= \frac{1}{2} (1 + 2 + 3) (20)^2 = 1200 \mu\text{J}.$$

**C-2.**

(a)  $C_{\text{eq}} = 0.4 \mu\text{F}$ ,

we connect five  $2 \mu\text{F}$  capacitors in series



$$\Rightarrow C_{\text{eq}} = \frac{C}{5} = \frac{2}{5} = 0.4 \mu\text{F}$$

(b)  $C_{\text{eq}} = 1.2 \mu\text{F}$ , capable of with standing 1000 volts


3 parallel rows, each consisting of five  $2.0 \mu\text{F}$  capacitors in series.

**C-3.**

There three circuit are equivalent and all these are balance wheat stone bridge. For all given circuits.

$$C_{\text{eq}} = \frac{5 \times 10}{5 + 10} + \frac{10 \times 20}{10 + 20} = 10 \mu\text{F} \quad \text{Ans.}$$

**C-4.**

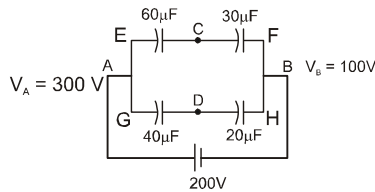

$$\text{Charge on } 30 \mu\text{F} = 200 \times 20 = 4000 \mu\text{C}$$

$$\text{so } V_C - V_B = \frac{4000 \mu\text{C}}{30 \mu\text{F}} \Rightarrow V_C = 100 + \frac{400}{3} = \frac{700}{3} \text{ V}$$

also charge on  $20 \mu\text{F}$


$$= 200 \times \frac{40}{3} = \frac{8000}{3} \mu\text{C}$$

$$\text{so अतः } V_D - V_B = \frac{8000/3}{20}$$

$$V_D = 100 + \frac{400}{3} = \frac{700}{3} \text{ V} \quad \Rightarrow \quad V_C - V_D = 0$$




C-5. Situation when S is open

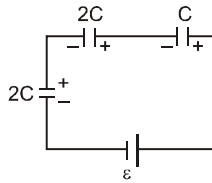

$$C_{eq} = C/2$$

$$\text{Charge supplied } Q = C_{eq} \cdot \varepsilon = \frac{C\varepsilon}{2}$$

Situation when S is closed

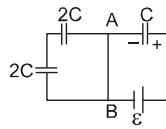

$$C_{eq} = C$$

$$\text{Charge on capacitor } C = C\varepsilon$$

After S is closed, voltage across 2C capacitor become zero, so charge on it also become zero.

(a) So charge flow through the battery when the switch S is closed =  $C\varepsilon - \frac{C\varepsilon}{2} = \frac{C\varepsilon}{2}$

(b) the charge flown through the switch S is  $\frac{C\varepsilon}{2} + \frac{C\varepsilon}{2} = C\varepsilon$  (A to B) =  $-C\varepsilon$  (B to A)

(c) Work done by the battery =  $Q_{supplied} V = \frac{C\varepsilon}{2} \cdot \varepsilon = \frac{C\varepsilon^2}{2}$


(d) change in energy stored in the capacitors

$$\text{energy stored in 2}^{nd} \text{ case} - \text{energy stored in 1}^{st} \text{ case} = \frac{1}{2} C_{eq2} V^2 - \frac{1}{2} C_{eq1} V^2 = \frac{1}{2} \cdot \left( C - \frac{C}{2} \right) \varepsilon^2 = \frac{C\varepsilon^2}{4}$$

(e) Heat developed in the system = Work done by battery – change in energy in the capacitors

$$= \frac{C\varepsilon^2}{2} - \frac{C\varepsilon^2}{4} = \frac{C\varepsilon^2}{4}$$

C-6. At steady state :

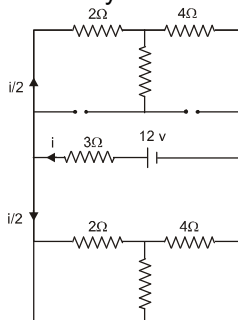

Current in wire AB at steady state =  $I/2 = 1$  amp.

Charge on  $2\mu\text{F}$  capacitor =  $2 \times 2 \times 10^{-6} = 4\mu\text{C}$

Charge on  $4\mu\text{F}$  capacitor =  $4 \times 4 \times 10^{-6} = 16\mu\text{C}$

Charge on  $6\mu\text{F}$  capacitor =  $2 \times 6 \times 10^{-6} = 12\mu\text{C}$

Charge on  $8\mu\text{F}$  capacitor =  $4 \times 8 \times 10^{-6} = 32\mu\text{C}$ .

### Section (D)

D-1.  $V = V_0(1 - e^{-t/RC})$

$$4 = 12(1 - e^{-1 \times 10^{-6} / 10C})$$

$$\ln \frac{3}{2} = \frac{10^{-7}}{C} \Rightarrow C = \frac{10^{-7}}{\ln 3/2} \text{ F} = 0.25 \mu\text{F}.$$





- D-2.** (i) (a) Time constant =  $t = RC = 10^7 \times 1 \times 10^{-6}$   
 = 10 sec.  
 (b)  $Q_0 = CV = 1 \times 10^{-6} \times 2 = 2 \mu\text{C}$   
 (c)  $Q = \frac{Q_0}{2} = Q_0(1 - e^{-t/RC})$   
 $t/RC = \ln 2 \Rightarrow t = 10 \ln 2 = 6.93 \text{ sec.}$   
 (ii)  $q = q_0 e^{-t/RC}$   
 =  $2 \times 10^{-6} e^{-50/10} = 2 \times 10^{-6} e^{-5} = 1.348 \times 10^{-8} \text{ C.}$

- D-3.** For charging  
 $q_1 = CV(1 - e^{-t/RC}) = 20 \times 10^{-4} (1 - e^{-16/200 \times 10^{-6} \times 40 \times 10^3}) = 20 \times 10^{-4} (1 - e^{-2})$   
 For discharging  
 $q_2 = q_1 e^{-t/RC}$   
 =  $20 \times 10^{-4} (1 - e^{-2})$   
 =  $20 \times 10^{-4} (1 - e^{-2}) e^{-2} = 20 \times 10^{-4} \frac{(e^2 - 1)}{e^4}$   
 =  $233.55 \mu\text{C}$  **Ans.**

- D-4.**  $i_0 = \frac{20}{5} \times \frac{1}{5} = \frac{4}{5} \text{ amp.}$   
 $i = i_0 e^{-t/RC}$   
 $H = \int i^2 R dt = \int_{25\mu\text{S}}^{50\mu\text{S}} \frac{16}{5} e^{-2t/25 \times 10^{-6}} dt$   
 =  $\frac{16}{5} \left( -\frac{25}{2} \times 10^{-6} \right) \left[ e^{-2t/25 \times 10^{-6}} \right]_{25\mu\text{S}}^{50\mu\text{S}}$   
 =  $40 \times 10^{-6} \left[ \frac{e^2 - 1}{e^4} \right]$   
 =  $4.7 \mu\text{J}$  **Ans.**

- D-5.** It can be seen that during the time interval from 0 to  $t_0$ , the voltage across the capacitor is zero, the charge on it is also zero, there is no current through it and hence  $V_{CD}$  is zero during this time interval (fig.). During the time interval from  $t_0$  to  $2t_0$ , the voltage across the capacitor and hence the charge on its plates, grows linearly and hence a direct current passes through the circuit. This means that the voltage  $V_{CD}$  is constant. During the time interval from  $2t_0$  to  $3t_0$ , the voltage across the capacitor does not change. Hence current does not flow, and  $V_{CD}$  is zero. Finally, during the time interval from  $3t_0$  to  $5t_0$ , the capacitor is discharged, the current through the resistor is negative and constant and its magnitude is half the value of the current during the time interval from  $t_0$  to  $2t_0$ .

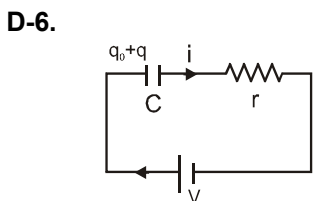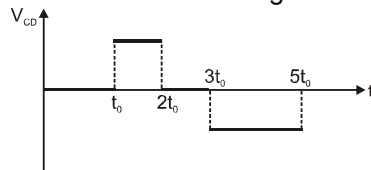

at time  $t$  using KVL

$$-\frac{q_0 + q}{C} - ir + V = 0 \Rightarrow -\frac{q_0 + q}{C} - \frac{dq}{dt} r + V = 0$$




$$\Rightarrow \int_0^q \frac{dq}{(CV - q_0) - q} = \int_0^t \frac{dt}{RC}$$

by using integration  $q = CV(1 - e^{-t/RC}) + q_0 e^{-t/RC} - q_0$

$$\Rightarrow \text{So charge on capacitor} = q_0 + q = CV(1 - e^{-t/RC}) + q_0 e^{-t/RC}$$

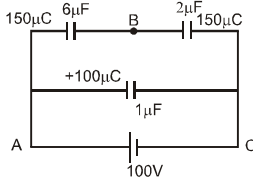D-7. In steady state equivalent circuit is



$$C_{eq} = \frac{5}{2} \mu F \quad Q = 250 \mu C$$

$$V_A = \frac{150}{6} + V_B \Rightarrow V_A - V_B = 25 \text{ V}$$

$$V_B = \frac{150}{2} + V_C \Rightarrow V_B - V_C = 75 \text{ V}$$

### Section (E)

E-1.  $V = \frac{Q}{C} = \frac{Q}{K \epsilon_0 \frac{A}{d}}; \quad R = \frac{\rho d}{A}$

(we can treat dielectric as a resistance between the capacitor plates)

$$i = \frac{V}{R} = \frac{Q}{K \epsilon_0 \frac{A}{d}} \cdot \frac{A}{\rho d} = \frac{Q}{K \epsilon_0 \rho} \quad \text{Ans}$$

E-2. (i)  $C_0 = \frac{\epsilon_0 A}{d} = \frac{0.2 \epsilon_0}{10^{-2}} = 20 \epsilon_0$   
 $= 20 \times 9 \times 10^{-12} = 180 \text{ pF}$

(ii)  $Q = C_0 V = 180 \times 10^{-12} \times 3000 = 5.4 \times 10^{-7} \text{ C}$

(iii)  $C_1 = \frac{Q}{V_1} = \frac{5.4 \times 10^{-7}}{1000} = 540 \text{ pF}$

(iv)  $K = \frac{C_1}{C_0} = \frac{540}{180} = 3$


(v)  $\epsilon = \epsilon_r \epsilon_0 = K \epsilon_0 = 3 \times 9 \times 10^{-12} = 27 \times 10^{-12} \text{ C}^2 \text{N}^{-1} \text{m}^{-2}$

(vi)  $E_0 = \frac{V}{d} = \frac{3000}{10^{-2}} = 3 \times 10^5 \text{ V/m}$

(vii)  $E = \frac{V_1}{d} = \frac{1000}{10^{-2}} = 1 \times 10^5 \text{ V/m}$



E-3.

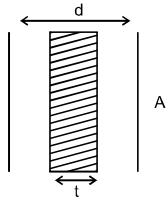

$$C' = \frac{A \epsilon_0}{\frac{t}{k} + d - t}$$

(i) Without dielectric,  $C = \frac{A \epsilon_0}{d}$

With dielectric,  $C' = \frac{A \epsilon_0}{\frac{t}{k} + d - t} = \frac{3C}{2} = \frac{3}{2} \frac{A \epsilon_0}{d} \Rightarrow \frac{d}{t} = \frac{2}{3}$

(ii) Energy =  $\frac{Q^2}{2C}$


Energy in 1<sup>st</sup> case =  $E_1 = \frac{q^2}{2C}$

Energy in 2<sup>nd</sup> case =  $E_2 = \frac{q^2}{2C'}$

$$\frac{E_1}{E_2} = \frac{C'}{C} = \frac{3}{2}$$

(iii)  $\Delta E = E_2 - E_1 = \frac{q^2}{2C'} - \frac{q^2}{2C} = \frac{q^2}{2} \left[ \frac{2}{3C} - \frac{1}{C} \right] = -\frac{q^2}{6C} = -\frac{q^2 d}{6A \epsilon_0}$

E-4.

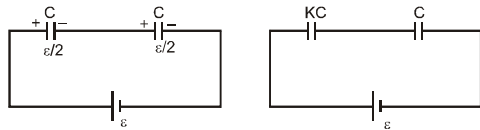

$$V_1 = \frac{Q_1}{kC} = \frac{\epsilon}{k+1} \Rightarrow E_1 = \frac{V_1}{d} = \frac{1}{k+1} \cdot \frac{\epsilon}{d} \Rightarrow E = \frac{Q}{dC} = \frac{\epsilon}{2d}$$

$$E_1 = \frac{2}{(k+1)} E \Rightarrow \frac{1}{2} (1+k) \text{ time decrease}$$

$$\Delta q = Q_1 - Q = \frac{kC\epsilon}{k+1} - \frac{C\epsilon}{2} = \frac{C\epsilon}{2(k+1)} (2k - k - 1) \Rightarrow \Delta q = \frac{1}{2} C\epsilon \frac{(k-1)}{(k+1)}$$

E-5. Work done on the system = change in potential energy

charge on plate =  $Q = CV = \frac{A \epsilon_0 V}{d}$

Initial potential energy =  $\frac{Q^2}{2C}$

where  $C = \frac{A \epsilon_0}{d}$

final potential energy =  $\frac{Q^2}{2C'}$


where  $C' = \frac{2KA \epsilon_0}{d}$

Change in potential energy = final potential energy – initial potential energy,

$$= \frac{Q^2}{2} \left\{ \frac{1}{C'} - \frac{1}{C} \right\} = \frac{\epsilon_0 AV^2}{2d} \left\{ \frac{1}{2K} - 1 \right\}$$



E-6.

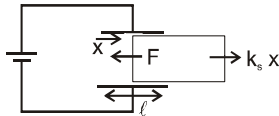

Potential energy =  $\frac{1}{2}(C_1 + C_2) V^2$

$$= \frac{1}{2} \left\{ \frac{\epsilon_0 x b}{d} + \frac{\epsilon_0 K(\ell - x)b}{d} \right\} V^2$$

$$F = -\frac{\partial U}{\partial x} = -\frac{V^2}{2} \frac{dC}{dx}$$

$$F = \frac{-1}{2} \frac{dC}{dx} V^2$$


where,  $\frac{dC}{dx} = \frac{\epsilon_0 b}{d} \{1 - K\}$

$$F = \frac{1}{2} \frac{V^2 \epsilon_0 b(K - 1)}{d}$$

at equilibrium,  $F = K_s x$

$$x = \frac{F}{K_s} = \frac{\epsilon_0 b V^2 (K - 1)}{2dK_s}$$

E-7.

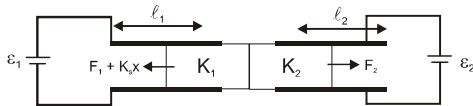

Force on dielectric  $F = \frac{\partial U}{\partial x} = -\frac{V^2}{2} \frac{dC}{dx}$

$$F = \frac{V^2 \epsilon_0 b(K - 1)}{2d}$$

At equilibrium

$$F_2 = F_1 + K_s x$$

$$x = \frac{\epsilon_0 b}{2dK_s} \left[ (K_2 - 1)\epsilon_2^2 - (K_1 - 1)\epsilon_1^2 \right]$$

E-8.

When dielectric slab is released from rest constant force act on slab towards the mean position after mean position same opposite force is act on slab which retard it come in rest position. Therefore motion of slab is periodic.

$$F = \frac{1}{2} \frac{\epsilon_0 2\ell}{b} (K - 1) V^2$$

$$a = \frac{\epsilon_0 \ell}{mb} (K - 1) V^2$$

by  $S = \frac{1}{2} (\text{acc.}) t^2$

$$(\ell) = \frac{1}{2} \frac{\epsilon_0 \ell}{mb} (K - 1) V^2 \cdot t^2$$


$$t = \sqrt{\frac{2\ell mb}{\epsilon_0 \ell (K - 1) V^2}}$$

$$\Rightarrow t = 2 \sqrt{\frac{mb}{\epsilon_0 (K - 1) V^2}} \Rightarrow T = 4t = 4 \sqrt{\frac{2bm}{\epsilon_0 V^2 (K - 1)}}$$






E-9. 1st part has di-electric;

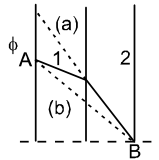

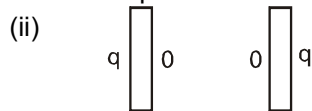(a) by  $E = \frac{Q}{A \epsilon_0}$  ; Q remain constant so electric field in region 1 varies same as region 2, so now electric field graph of obtain by extend E of region 2  
 (b) now V is constant so by  $E = V/D$  ; electric field graph directly obtain by joining A and B.

E-10. (i)  $C = \frac{\epsilon_0 A}{d}$   
 Capacitance is independent of charge stored



on outer surfaces charge =  $\frac{Q_1 + Q_2}{2} = \frac{q + q}{2} = q$

on inner surfaces charge =  $\frac{Q_1 - Q_2}{2} = \frac{q - q}{2} = 0$

- (iii)  $E = 0$   
 electric field due to charges on outer surfaces cancel each other
- (iv)  $\Delta V = 0$   
 because electric field between the plates is zero
- (v)  $U = 0$   
 because electric field between the plates is zero

## PART - II

### Section (A)

A-1.  $Q_t = Q_1 + Q_2 = 150 \mu\text{C}$

$$\frac{Q_1'}{Q_2'} = \frac{C_1}{C_2} = \frac{1}{2} \Rightarrow Q_1' = 50 \mu\text{C}$$

$$Q_2' = 100 \mu\text{C}$$

25  $\mu\text{C}$  charge will flow from smaller to bigger sphere.

A-2. Charge is flow until potential are equal and in charge flow energy is decrease

$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2} \Rightarrow Q_1 R_2 = Q_2 R_1 .$$

A-3. (i) (C)  $E = \frac{V}{d} = \frac{300}{2.5 \times 10^{-2}} = 12 \times 10^3 \text{ V/m}$

(ii) (D)  $\Delta U = U_f - U_i = \frac{1}{2} C_f V^2 - \frac{1}{2} C_i V^2$

$$= \frac{1}{2} \left( \frac{\epsilon_0 A}{d_f} - \frac{\epsilon_0 A}{d_i} \right) V^2$$

$$= \frac{1}{2} \left( \frac{1}{2.5} - \frac{1}{2} \right) \frac{9 \times 10^{-12} \times 100 \times 10^{-4}}{10^{-2}} (300)^2 = -405 \times 10^{-10} \text{ J} .$$



(iii) (D)  $E = \frac{Q}{A \epsilon_0} = \text{Constant}$   
 $= \frac{V}{d_i} = \frac{300}{2 \times 10^{-2}} = 15 \times 10^3 \text{ V/m.}$

(iv) (C)  $Q = \frac{A \epsilon_0}{d_i} V = \text{constant}$

$$\Delta U = \frac{1}{2} \frac{Q^2}{C_f} - \frac{Q^2}{C_i} = \frac{1}{2} A \epsilon_0 V^2 \left( \frac{d_f}{d_i^2} - \frac{d_i}{d_i^2} \right)$$

$$= \frac{1}{2} \frac{A \epsilon_0}{d_i^2} V^2 (d_f - d_i) = \frac{1}{2} \frac{100 \times 10^{-4} \times 9 \times 10^{-12} \times (300)^2 (2.5 - 2) \times 10^{-2}}{(2 \times 10^{-2})^2} = 5.0625 \times 10^{-8} \text{ J Ans.}$$

- A-4. (B) Isolated capacitor  $\Rightarrow Q = \text{constant}$   
 separation  $d$  increase  $\Rightarrow C = \text{decrease}$   
 $Q = CV \Rightarrow V = \text{increase}$


A-5. The charge on the capacitor remains constant

Capacitance  $C = \frac{\epsilon_0 A}{d} \quad d \uparrow \quad C \downarrow$   
 Energy  $U = \frac{1}{2} \frac{Q^2}{C} \quad C \downarrow \quad U \uparrow$   
 Potential  $V = \frac{Q}{C} \quad C \downarrow \quad V \uparrow$

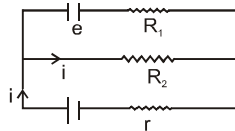**Section (B)**

B-1.  $W = U_f - U_i = \frac{1}{2} C V_f^2 - \frac{1}{2} C V_i^2 = \frac{1}{2} C (40^2 - 20^2) \quad W = 600 \text{ C}$   
 $W_1 = \frac{1}{2} C (50^2 - 40^2) = \frac{900}{2} \text{ C}$   
 $W_1 = \frac{900}{2} \cdot \frac{W}{600} = \frac{3}{4} W \quad \text{Ans}$

- B-2. Charge on capacitor =  $CV = \text{capacitance} \times (\text{voltage across it})$   
 In steady state, there will be no current through capacitor.



voltage across capacitor  $V = iR_2 = \frac{E R_2}{R_2 + r}$

Charge on capacitor =  $CiR_2 = \frac{C E R_2}{R_2 + r}$

- B-3. As battery is disconnected, charge remains constant in the work process.  
 Work done = final potential energy – initial potential energy


$$= \frac{Q^2}{2 C'} - \frac{Q^2}{2 C} = \frac{Q^2}{2} \left\{ \frac{1}{C'} - \frac{1}{C} \right\}$$

Where,  $Q = CV = \frac{A \epsilon_0 V}{d}, \quad C = \frac{A \epsilon_0}{d} \quad \& \quad C' = \frac{A \epsilon_0}{2 d}$

Now, work done =  $\frac{\epsilon_0 AV^2}{2d} \quad \text{Ans. is (D)}$




B-4.

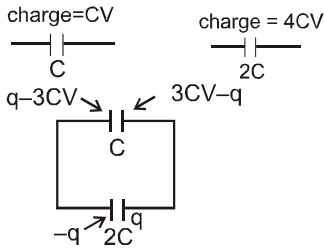

Total charge =  $4 CV - CV = 3 CV$

Now, let it is distributed as shown, potential across the capacitors is same

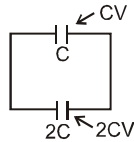
$$\text{So, } \frac{q}{2C} = \frac{3CV - q}{C} \Rightarrow q = 2 CV$$



$$\text{Total potential energy} = \frac{Q_1^2}{2C_1} + \frac{Q_2^2}{2C_2} = \frac{C^2 V^2}{2C} + \frac{4C^2 V^2}{2 \times 2C} = \frac{3CV^2}{2}$$

B-5. Common potential

$$V = \frac{V_0 C + 0}{C + C_x}$$

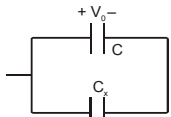

$$V (C + C_x) = V_0 C$$


$$C + C_x = \frac{V_0}{V} C$$

$$C_x = C$$

$$C_x = \frac{C(V_0 - V)}{V}$$


### Section (C)

C-1.

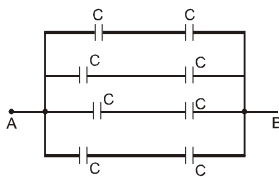

$$C_{eq} = \frac{4C}{2} = 2C.$$

C-2.

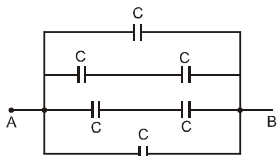


$$C_{eq} = C + 2C/2 + C = 3C.$$




**C-3.**  $\frac{1}{C_1} = \frac{1}{3} + \frac{1}{3} + \frac{1}{3}$

$\Rightarrow C_1 = 1 \mu\text{F}, C_2 = 2 + 1 = 3 \mu\text{F}$   
 $C_{\text{eq}} = 1 \mu\text{F}.$


**C-4.**

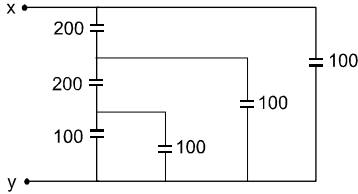


$\Rightarrow$

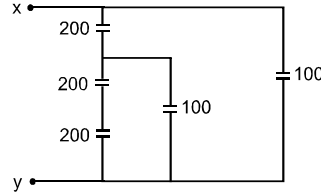


solving by parallel series combinations,

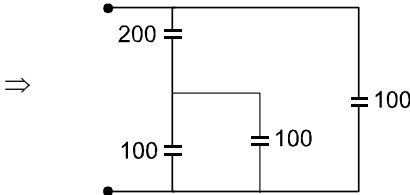


$\Rightarrow$

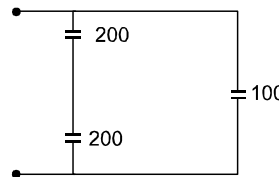


$\Rightarrow$

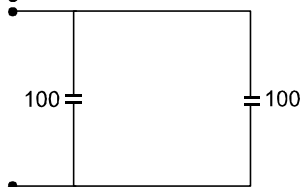

$\Rightarrow$

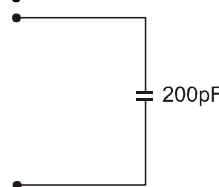

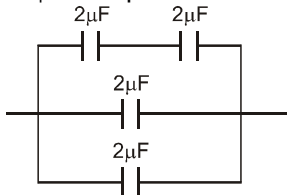
$C_{\text{eq}} = 200 \text{ pF}$  **Ans.**



**C-5.**

Minimum 4 capacitors required as shown in figure

**C-6.**

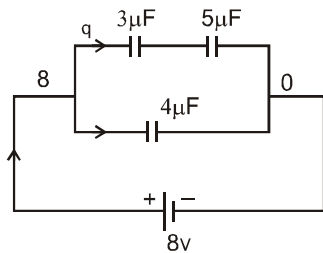

$C_{\text{eq}} = \frac{15}{8} + 4 = \frac{47}{8} \mu\text{F}$


$\frac{q}{3} + \frac{q}{5} = 8 \Rightarrow q = 15 \mu\text{C}$

Charge on  $2 \mu\text{F}$

$\frac{q_1}{2} = \frac{15 - q_1}{3} \Rightarrow q_1 = \frac{30}{5} = 6.0 \mu\text{C}$  **Ans.**




C-7.

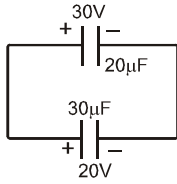

$$\text{Common potential } V = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} = \frac{600 + 600}{20 + 30} = 24 \text{ V}$$


C-8.

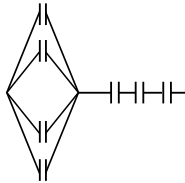

$$\frac{1}{C_{eq}} = \frac{1}{8} + \frac{1}{2} + \frac{1}{2} + \frac{1}{2}$$


$$= \frac{1}{8} + \frac{3 \times 4}{2 \times 4}$$
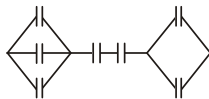
$$\frac{1}{C_{eq}} = \frac{13}{8} \Rightarrow C_{eq} = \frac{8}{13} \mu\text{F}$$




$$\frac{1}{C_{eq}} = \frac{1}{6} + \frac{1}{2} + \frac{1}{2} + \frac{1}{4}$$
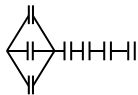
$$\frac{1}{C_{eq}} = \frac{17}{12} \Rightarrow C_{eq} = \frac{12}{17} \mu\text{F}$$



$$\frac{1}{C_{eq}} = \frac{1}{6} + \frac{1}{2} \times 4$$
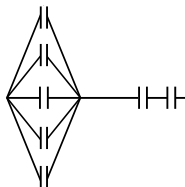
$$\frac{1}{C_{eq}} = \frac{13}{6} \Rightarrow C_{eq} = \frac{6}{13} \mu\text{F}$$



$$\frac{1}{C_{eq}} = \frac{1}{10} + \frac{1}{2} + \frac{1}{2}$$

$$\frac{1}{C_{eq}} = \frac{10}{11} \mu\text{F}$$

**Section (D)**

D-1. (i) (C)  $q_0 = 4 \mu\text{C}$

$$i = \frac{dq}{dt} = \frac{q_0}{RC} e^{-t/RC} = \frac{4 \times 10^{-6}}{1 \times 10^{-6} \times 3 \times 10^6} e^{-1/3} = \frac{4}{3} e^{-1/3} \mu\text{C/sec}$$

(ii) (A)  $U = \frac{q_0^2}{2C} (1 - e^{-t/RC})^2$

$$\frac{dU}{dt} = \frac{q_0^2}{RC^2} (1 - e^{-t/RC}) e^{-t/RC}$$

$$= \frac{(4 \times 10^{-6})^2}{3 \times 10^6 \times (1 \times 10^{-6})^2} (1 - e^{-1/3}) e^{-1/3} = 16/3 (1 - e^{-1/3}) e^{-1/3} \mu\text{J/sec.}$$



(iii) (C)  $H = \int i^2 R dt \Rightarrow \frac{dH}{dt} = i^2 R$

$$\frac{dH}{dt} = i_0^2 R e^{-2t/RC} = \left( \frac{4}{3 \times 10^6} \right)^2 3 \times 10^6 e^{-2/3} = 16/3 e^{-2/3} \mu J / s$$


(iv) (C)  $U = qV \Rightarrow \frac{dU}{dt} = V \frac{dq_0}{dt} (1 - e^{-t/RC})$

$$\begin{aligned} \frac{dU}{dt} &= \frac{q_0 V}{RC} e^{-t/RC} \\ &= \frac{4 \times 10^{-6} \times 4}{3 \times 10^6 \times 1 \times 10^6} e^{-1/3} = \frac{16}{3} e^{-1/3} \mu J / sec. \end{aligned}$$

D-2. (i) (A)  $i_0 = \frac{V}{R} = \frac{6}{24} = 0.25 \text{ A}$

(ii) (B)  $i = i_0 e^{-t/RC}$   
 $= 0.25 e^{-1}$   
 $= \frac{0.25}{e} = 0.09 \text{ A.}$

D-3.

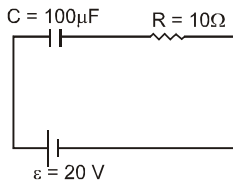

Energy stored in capacitor  $= \frac{Q^2}{2 C}$

Rate at which energy is stored  $= \frac{d}{dt} \left( \frac{Q^2}{2 C} \right) = \frac{Q}{C} \cdot \frac{dQ}{dt} = \frac{Qi}{C}$

$Q = \epsilon C \{1 - e^{-t/RC}\}$

$i = \frac{\epsilon e^{-t/RC}}{R}$

Rate of energy storage  $= \frac{\epsilon^2}{R} \{1 - e^{-t/RC}\} \{e^{-t/RC}\} = \frac{\epsilon^2}{R} \{e^{-t/RC} - e^{-2t/RC}\} \dots\dots\dots (1)$

It will be maximum when,  $e^{-t/RC} - e^{-2t/RC}$  will be maximum let  $y(t) = e^{-t/RC} - e^{-2t/RC}$   
 for maximum ,  $y'(t) = 0$

$$y'(t) = \frac{-e^{-t/RC}}{R C} + \frac{2 e^{-2t/RC}}{R C}$$

$$e^{-t/RC} = \frac{1}{2}$$

Putting it back in eq. (1)

(i) Maximum rate of energy storage

$$= \frac{\epsilon^2}{R} \left\{ \frac{1}{2} - \left( \frac{1}{2} \right)^2 \right\} = \frac{\epsilon^2}{4 R} = \frac{(20)^2}{4 \times 10} = 10 \text{ J/s} \quad \text{Ans. is (A)}$$

(ii) This will occur when,  $e^{-t/RC} = 1/2$

$$\frac{-t}{RC} = \ln \frac{1}{2}$$


$t = RC \ln 2 = 10 \times 100 \times 10^{-6} \times \ln 2 = (\ln 2) \text{ ms} \quad \text{Ans. is (C)}$



D-4.  $q = \frac{q_1}{2} = \frac{8 \times 10^{-6} \times 10}{2} \left( 1 - e^{-\frac{0.16 \times 10^{-3}}{8 \times 10^{-6} \times 20}} \right)$   
 $q = 40(1 - e^{-1}) \mu\text{C} = 40(1 - 0.37) = 25.2 \mu\text{C}$       **Ans.**


- D-5. (i) **(B)** at  $t_0$ ;  $q = q_0 = 60 \mu\text{C}$   
 (ii) **(C)**  $q = q_0 e^{-t/RC} = 60 \times 10^{-6} e^{-100 \times 10^{-6} / 10 \times 10^{-6} \times 10} = \frac{60}{e} \mu\text{C} = 22 \mu\text{C}$ .  
 (iii) **(A)**  $q = q_0 e^{-t/RC} = 60 \times 10^{-6} e^{-1 \times 10^{-3} / 10 \times 10^{-6} \times 10} = \frac{60}{e^{10}} \mu\text{C} = 0.003 \mu\text{C}$ .

D-6. (C)

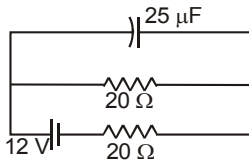

Switch is kept closed for a long time,  
 Current through  $20\Omega$  resistor  $i = \frac{12}{40}$   
 Charge on the capacitor at steady state,  
 $q_0 = 25 \times \frac{12}{40} \times 20 = 150 \mu\text{C}$

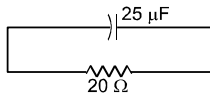
at  $t = 0$ , switch is opened,  $i = i_0 e^{-t/\tau}$   
 $\tau = RC = 20 \times 25 = 500 \mu\text{s}$



Current  $i = \frac{q_0}{\tau} e^{-\frac{0.25 \times 10^{-3}}{500 \times 10^{-6}}}$   
 $i = \frac{150}{500} e^{-1/2} = 0.189 \text{ A}$

D-7. If  $S_1$  is closed and  $S_2$  is open then, condenser C is fully charged at potential V.

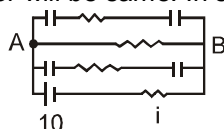D-8. Charge on each capacitor will be same. In steady state current through capacitor will be zero



current in steady state  $= i = 10/5 = 2 \text{ amp}$   
 potential across  $AB = iR = 2 \times 4 = 8 \text{ V}$ .  
 Potential across each capacitor  $= 4 \text{ V}$   
 on each plate  $Q = CV = 3 \times 4 = 12 \mu\text{C}$

D-9.  $\frac{q_1}{C_1} = \frac{q_2}{C_2}$

$\frac{I_1}{C_1} = \frac{I_2}{C_2}$        $C_1 = C_2$

$I = I_1 + I_2$

$I_1 = \frac{IC_1}{C_1 + C_2}$



**Section (E)**

E-1.  $C' = \frac{\epsilon_0 A}{d/2} = \frac{2\epsilon_0 A}{d} = 2C.$


E-2.  $Q = \text{constant}$   
New capacitance =  $KC$  (increases)

$V' = \frac{V}{K}$  (decreases)

$U' = \frac{Q^2}{2CK}$  (decreases)

$E = \frac{Q}{A\epsilon_0} \Rightarrow E' = \frac{Q}{KA\epsilon_0}$  (decreases)

E-3.

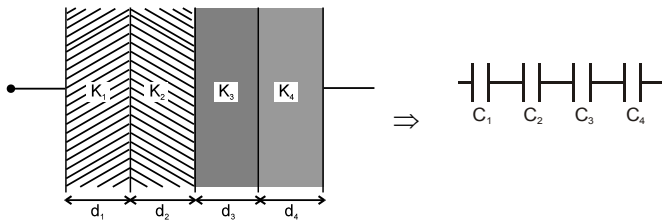

$C_1 = \frac{K_1\epsilon_0 A}{d_1}, C_2 = \frac{K_2\epsilon_0 A}{d_2}, C_3 = \frac{K_3\epsilon_0 A}{d_3}, C_4 = \frac{K_4\epsilon_0 A}{d_4}$

$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4}$

$\frac{1}{C_{eq}} = \frac{d_1}{K_1\epsilon_0 A} + \frac{d_2}{K_2\epsilon_0 A} + \frac{d_3}{K_3\epsilon_0 A} + \frac{d_4}{K_4\epsilon_0 A}$

$C_{eq} = \frac{\epsilon_0 A}{\left[ \frac{d_1}{K_1} + \frac{d_2}{K_2} + \frac{d_3}{K_3} + \frac{d_4}{K_4} \right]}$

E-4.  $V_{C_2} = V_{C_2} = V$

$C_1 = C$


$C_2 = KC$

$q_1 = C_1 V_{C_1} = CV$

$q_2 = C_2 V_{C_2} = KCV$

$q_1 < q_2.$

E-5.

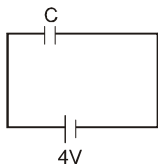

Here, Potential difference on the capacitor will depend on emf of battery i.e.,  $4V$  (C)

E-6. Charge on battery =  $Q = CV = 4C$

Now charge remains same, as battery is disconnected new capacitance =  $C' = KC = 8C$

$C'V' = Q \quad V' = \frac{Q}{C'} = \frac{4C}{8C} = \frac{1}{2} V \quad (A)$





**E-7.**  $U_0 = \frac{1}{2} CV^2$  (given)      Now energy =  $U' = \frac{1}{2} C' V^2$   
 $C' = CK$   
 $U' = \frac{1}{2} CV^2 K = U_0 K$       **Ans. is (A)**

**E-8.** Now, charge remains same on the plates.

$$U_0 = \frac{Q^2}{2C} \text{ (given)}$$

$$\text{Now energy} = U' = \frac{Q^2}{2C'} = \frac{Q^2}{2CK} = \frac{U_0}{K} \text{ (C) Ans}$$

**PART - III**

- 1.** The initial charge on capacitor =  $CV_i = 2 \times 1 \mu C = 2 \mu C$   
 The final charge on capacitor =  $CV_f = 4 \times 1 \mu C = 4 \mu C$   
 $\therefore$  Net charge crossing the cell of emf 4V is  
 $q_f - q_i = 4 - 2 = 2 \mu C$   
 The magnitude of work done by cell of emf 4V is  
 $W = (q_f - q_i) 4 = 8 \mu J$   
 The gain in potential energy of capacitor is  
 $\Delta U = \frac{1}{2} C(V_f^2 - V_i^2) = \frac{1}{2} \times 1 \times [4^2 - 2^2] \mu J = 6 \mu J$   
 Net heat produced in circuit is  
 $\Delta H = \frac{1}{2} C(V_f^2 - V_i^2) W - \Delta U = 8 - 6 = 2 \mu J$

**SECTION (D)**

- 2.** (A) For potential difference across each cell to be same

$$E_1 - ir = E_2 + ir \quad \text{or} \quad i = \frac{E_1 - E_2}{2r} \left( < \frac{E_1 - E_2}{2r + R} \right)$$

Hence potential difference across both cells cannot be same.

Cell of lower emf charges up.

For potential difference across cell of lower emf to be zero

$$E_2 + ir = 0 \text{ which is not possible.}$$

Current in the circuit cannot be zero  $\because E_1 \neq E_2$ .

- (B) For potential difference across each cell to be same

$$E_1 - ir = E_2 - ir \text{ which is not possible}$$

No cell charges up.

For potential difference across cell of lower emf to be zero

$$E_2 - ir = 0 \quad \text{and} \quad E_1 - i(r + R) = 0$$

$$\text{or} \quad \frac{E_1}{r + R} = \frac{E_2}{r} \text{ which is possible. } \therefore E_1 > E_2.$$

Current in the circuit cannot be zero.

- (C) Situation is same as in (A) except current decreases from  $\frac{E_1 - E_2}{2r + R}$  to zero.

Hence the only option that shall changes is 'current shall finally be zero.'

- (D) Situation is same as in (B) except current decreases from  $\frac{E_1 + E_2}{2r + R}$  to zero.


Hence the only option that shall changes is 'current shall finally be zero.'




## EXERCISE -2 PART - I

1.  $x = Vt \Rightarrow d \propto t \quad C = \frac{\epsilon_0 A}{Vt} \quad \frac{dc}{dt} = -\frac{\epsilon_0 A}{V} \frac{1}{t^2} \quad \frac{dc}{dt} \propto \frac{1}{d^2} \quad \text{Ans}$

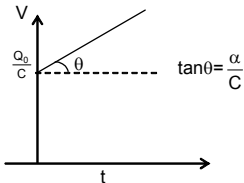
2. Given  $Q = (\alpha t + Q_0)$   
 $V = \frac{Q}{C} = \frac{\alpha t + Q_0}{C} = \frac{\alpha t}{C} + \frac{Q_0}{C}$



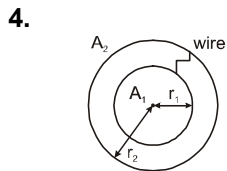3. Theoretical capacitance =  $\infty$ , because d become zero



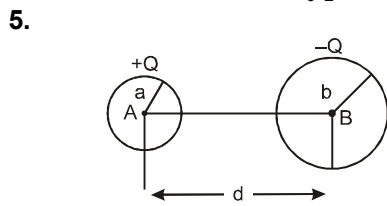All given charge of  $A_1$  goes to  $A_2$   
 Therefore  $C = 4\pi\epsilon_0 r_2$



$$V_B = \frac{KQ}{d} - \frac{KQ}{b}$$

$$V_A = \frac{KQ}{a} - \frac{KQ}{d}$$

$$V_A - V_B = KQ \left[ \frac{1}{a} + \frac{1}{b} - \frac{2}{d} \right]$$

$$= \frac{Q}{4\pi\epsilon_0} \left[ \frac{1}{a} + \frac{1}{b} - \frac{2}{d} \right]$$

or  $\frac{Q}{V_A - V_B} = C = \frac{4\pi\epsilon_0}{\left( \frac{1}{a} + \frac{1}{b} - \frac{2}{d} \right)}$




6. Charge on  $C_0$ ,  $Q_1 = C_0V_0$ ,  
Initial charge on  $C_1$ ,  $Q_2 = 0$

$$\text{Common potential } V_1 = \frac{Q_1 + Q_2}{C_1 + C_2} = \frac{C_0V_0}{C + C_0} \Rightarrow Q_1 = C_0V_1 = \frac{C_0^2}{C + C_0} V_0$$

Similarly  $V_2 = \frac{C_0V_1}{C + C_0} = \left(\frac{C_0}{C + C_0}\right)^2 V_0 \Rightarrow Q_2 = C_0V_2 = \frac{C_0^3}{(C + C_0)^2} V_0$


for n times  $V_n = \left(\frac{C_0}{C + C_0}\right)^n V_0 = V \Rightarrow C = \left[\left(\frac{V_0}{V}\right)^{1/n} - 1\right] C_0$  **Ans**

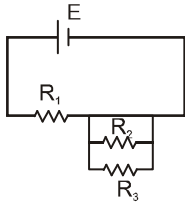7. Immediately after the key is closed, capacitor behave like a conducting wire, therefore.




$$i = \frac{E}{R_1}$$
 **Ans**

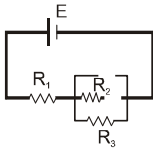After a long time interval, capacitor behave like an open circuit. Therefore.




$$i = \frac{E}{R_1 + R_3}$$
 **Ans**


- 8.

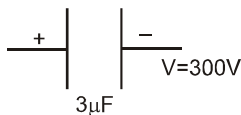


$$Q_1 = C_1V_1 = 900\mu\text{C}$$

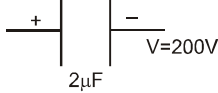

$$Q_2 = C_2V_2 = 400\mu\text{C}$$

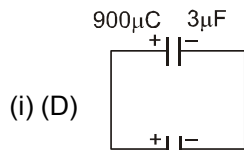
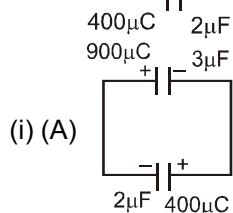
$$V = \frac{Q_1 + Q_2}{C_1 + C_2} = \frac{900 + 400}{3 + 2} = 260\text{V}$$




$$V = \frac{Q_1 + Q_2}{C_1 + C_2} = \frac{900 - 400}{3 + 2} = 100\text{V}$$

Charge on  $3\mu\text{F} = C_1V = 300\mu\text{C}$

amount of charge flow is  $= 900\mu\text{C} - 300\mu\text{C} = 600\mu\text{C} = 6 \times 10^{-4} \text{C}$





9. Just after switch closing

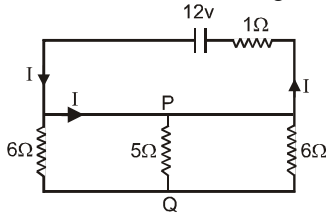

current through resistor PQ is zero just after closing the switch.

10.

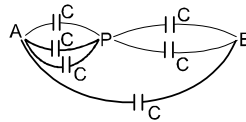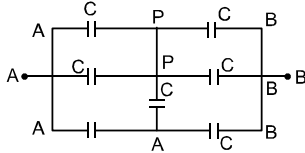


Get


$$C_{eq} = \frac{11c}{5}$$

$$\text{Charge flow} = C_{eq} \varepsilon = \frac{11 C \varepsilon}{5}$$

11.

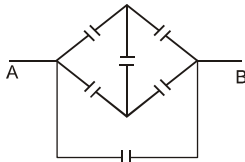

≡

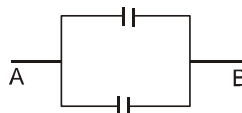

$$C_{eq} = 2C$$


12.

$$(i) \frac{1}{C_1'} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\Rightarrow C_1' = 1\mu F$$

$$C_2' = C_2 + C_1' = 3\mu F \Rightarrow C_{eq} = 1\mu F$$

Ans

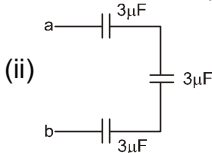


$$C_{eq} = 1\mu F \quad Q = C_{eq} V = 900\mu F$$

charge on nearest capacitor =  $900\mu F$

Ans

(iii) from point potential method

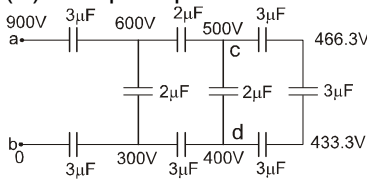


$$V_c - V_d = 100V$$

Ans





13.

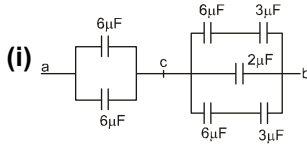

$$C_{ac} = 6 + 6 = 12\mu\text{F} \quad C_{cb} = 2\left(\frac{6.3}{6+3}\right) + 2 = 6\mu\text{F}$$


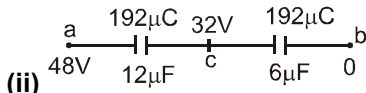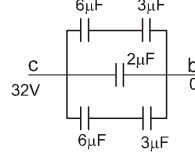
$$C_{eq} = \frac{12 \times 6}{12 + 6} = 4\mu\text{F} \quad \text{Ans}$$




Charge on  $2\mu\text{F}$  capacitor  $\Rightarrow$

$$Q = CV \quad Q = 2 \times 32 = 64\mu\text{C}$$


Ans

14.

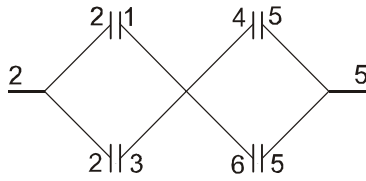

$$C_{eq} = \frac{C}{2} + \frac{C}{2} = C = \frac{\epsilon_0 A}{d} \quad \text{Ans.}$$


15.

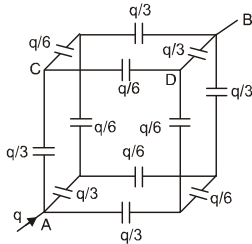

Due to symmetric charge distribution as shown for loop ACDB

$$V_A - \frac{q}{3C} - \frac{q}{6C} - \frac{q}{3C} = V_B \quad \Rightarrow \quad V_A - V_B = \frac{5q}{6C} \quad \Rightarrow \quad V_A - V_B = \frac{q}{C_{eq}} \quad \Rightarrow \quad C_{eq} = \frac{6C}{5} \quad \text{Ans}$$

16.

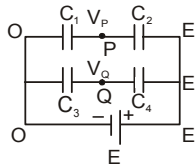

$C_1$  and  $C_2$  are in series, charge on each will remain same.

$$(V_P - 0) \cdot C_1 = (E - V_P) C_2$$

$$V_P = \frac{C_2 E}{C_1 + C_2}$$

$C_3$  &  $C_4$  are in series, charge on each will remain same,


$$(V_Q - 0) \cdot C_3 = (E - V_Q) \cdot C_4$$

$$V_Q = \frac{C_4 E}{(C_3 + C_4)}$$

$$\text{Hence } V_P - V_Q = \frac{(C_2 C_3 - C_1 C_4) E}{(C_1 + C_2) (C_3 + C_4)}$$




17.

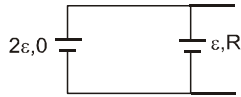



$$\Rightarrow E = \frac{\frac{E_1}{r_1} + \frac{E_2}{r_2}}{\frac{1}{r_1} + \frac{1}{r_2}} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2} = \frac{2\epsilon R + \epsilon \times 0}{0 + R}$$
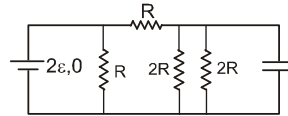
$$\Rightarrow E = 2\epsilon, r_{eq} = \frac{r_1 r_2}{r_1 + r_2} = 0$$



Equivalent battery

$$i_{max} = \frac{2\epsilon}{R}$$

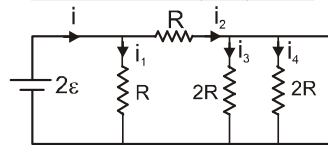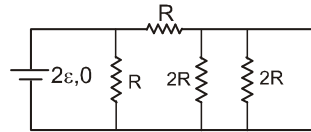

for  $Q_{max} \Rightarrow$

$$i = \frac{2\epsilon}{2R/3} = \frac{3\epsilon}{R} \quad i_2 = \frac{\epsilon}{R}, \quad i_1 = \frac{2\epsilon}{R}, \quad i_3 = i_4 = \frac{\epsilon}{2R}$$


potential on C = potential on 2R resistance =  $i_3 \times 2R = \epsilon$

charge on capacitor,  $Q_{max} = CV = C\epsilon$

$$\tau = \frac{Q_{max}}{i_{max}} = \frac{C\epsilon}{2\epsilon/R} = \frac{RC}{2}$$

Ans

18.

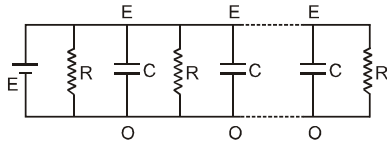

$$Q_{first} = Q_{last} = CE$$

$$\text{Ratio} = \frac{Q_{first}}{Q_{last}} = 1.$$

19.

From the given conditions, resistance of analog voltmeter = 10 kΩ

$$\text{Initial current} = \frac{1.5}{10} \text{ mA}$$

$$= \frac{1500}{10} \mu\text{A} = 150 \mu\text{A}$$

$$\text{Using, } 0.5 = 1.5 e^{-t/RC} = 1.5 e^{-t/10}$$


$$\frac{1}{3} = e^{-\frac{t}{10}}$$

$$\ln 3 = t$$

$$t = \ln 3$$



20. (A)

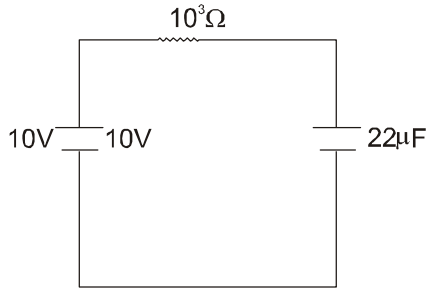

$RC = 10^3 \times 22 \times 10^{-6}$   
 $RC = 10^3 \times 22 \times 10^{-6} = 22 \times 10^{-3} \text{ sec}$   
 At  $t = 1.5 \text{ sec}$   
 steady state  $V_C = 10V$


While discharging  $V = 10e^{\frac{-t \times 10^3}{15}} = 1.226$

$$e^{\frac{10^3 t}{15}} = 0.1226$$

$$t = \frac{-15}{100} \ln(0.1226)$$

= 330 ms.

21

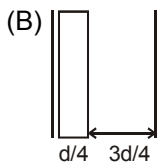


Capacitance of capacitor without dielectric,  $C_0 = \frac{\epsilon_0 A}{d}$

Capacitance of capacitor with dielectric, C

$$C = \frac{\epsilon_0 A}{\frac{3d}{4} + \frac{d}{4\epsilon_r}} = \frac{4\epsilon_0 A \cdot \epsilon_r}{((3\epsilon_r + 1)d)} \Rightarrow \frac{C}{C_0} = \frac{4\epsilon_r}{(3\epsilon_r + 1)}$$

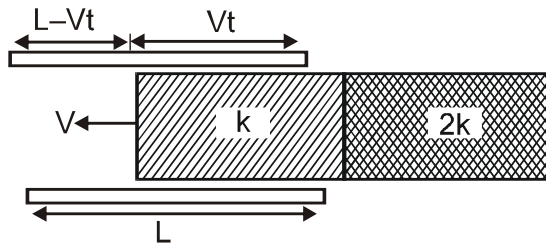22. Case – I When dielectric slab of dielectric constant K enters in to the capacitor.



At any time t, there will be two capacitors are in parallel combination - one with air and other with dielectric slab.

$$C(t) = C_{\text{air}} + C_{\text{slab}}$$


$$= \frac{\epsilon_0 A (L - Vt)}{Ld} + \frac{K \epsilon_0 A (Vt)}{Ld}$$

$$= \frac{\epsilon_0 A}{Ld} [L - (K - 1) Vt] \text{ (linear function of } t \text{)}$$

Its slope =  $M C(t) = \frac{\epsilon_0 A}{Ld} (K - 1) V$



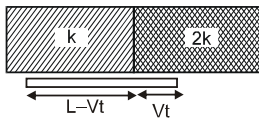**Case – II** When dielectric slab of dielectric constant  $2K$  also enters into the capacitor.



$$C'(t) = C_{\text{slab 1}} + C_{\text{slab 2}}$$


$$= \frac{\epsilon_0 AK (L - Vt)}{Ld} + \frac{\epsilon_0 A2K Vt}{Ld}$$

$$= \frac{K \epsilon_0 A}{Ld} [L + Vt] \quad (\text{linear function of } t)$$

Its slope =  $MC'(t) = \frac{\epsilon_0 AKV}{Ld}$

As =  $M C'(t) > MC(t)$

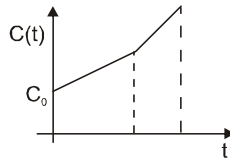and both  $C(t)$  and  $C'(t)$  are linear function of 't' hence variation of capacitance with time be best represented by (B)



23.  $U = \frac{Q^2}{2C}$  since C will become k times

So U will become  $\frac{1}{k}$  times

24.

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{\frac{A\epsilon_0}{d} + \frac{KA\epsilon_0}{d}}$$


$$= \frac{d}{2A\epsilon_0} + \frac{d}{2KA\epsilon_0}$$

$$\frac{1}{C_{\text{eq}}} = \frac{d}{2A\epsilon_0} \left( \frac{K+1}{K} \right)$$

$$C_{\text{eq}} = \frac{2KA\epsilon_0}{d(K+1)}$$

$$\frac{C_{\text{eq}}}{C_{\text{eq}'}} = \frac{2KA\epsilon_0}{d(K+1)} \cdot \frac{2d}{A\epsilon_0(K+1)} = \frac{4K}{(K+1)^2}$$

25. Rearrange the circuit

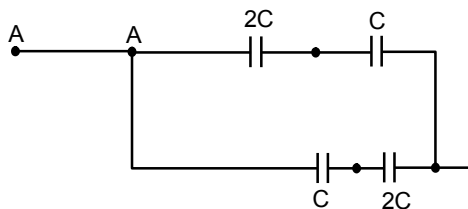

$$C_{\text{eq}} = \frac{2C}{3} \times 2$$





**PART - II**

1.  $C_{eq}$  can be written as  $C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{a^2 \epsilon_0}{3d}$


charge on plate  $Q = C_{eq}V = \frac{a^2 \epsilon_0 V}{3d}$

surface charge density  $= \sigma = \frac{Q}{a^2} = \frac{\epsilon_0 V}{3d}$

electric field  $= \frac{\sigma}{2\epsilon_0} + \frac{\sigma}{2\epsilon_0} = \frac{\sigma}{\epsilon_0} = \frac{V}{3d}$

electric force  $= \frac{Ve}{3d}$

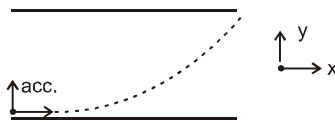acceleration of electrons  $= \frac{Ve}{(3d)m}$



in X axis  $a = ut$   $t = \frac{a}{u}$

in Y axis  $\Rightarrow \frac{1}{2} \times \text{acceleration} \times t^2 = d$

$\frac{Vet^2}{2(3d)m} = d$   $\frac{Vea^2}{6dmu^2} = d$

$u = \left\{ \frac{Vea^2}{6md^2} \right\}^{\frac{1}{2}}$

2.  $C_{eq} = \frac{2C}{3}$

$Q = \frac{2CV}{3}$

surface charge density  $= \sigma = \frac{Q}{A} = \frac{2CV}{3A}$

Electric field between the plates of capacitor

$= \frac{\sigma}{2\epsilon_0} + \frac{\sigma}{2\epsilon_0} = \frac{\sigma}{\epsilon_0} = \frac{2CV}{3A\epsilon_0}$

Force बल  $= qE = \frac{2CVq}{3A\epsilon_0}$

for equilibrium this electrostatic force must be equal to  $mg \Rightarrow \frac{2CVq}{3A\epsilon_0} = mg$

$V = \frac{3mgA\epsilon_0}{2Cq}$



3.  $Q = CV = 2 \times 12 = 24\mu\text{C}$   
 $\frac{Q_1}{Q_2} = \frac{C_1}{C_2} = \frac{1}{2}$ ,  $Q_1 + Q_2 = 24\mu\text{C}$ ,  $V = \frac{Q_1 + Q_2}{C_1 + C_2} = 4 \text{ Volt}$

(a)  $Q_1 = 8\mu\text{C}$ ,  $Q_2 = 16\mu\text{C}$   
 initial charge on  $4\mu\text{F} = 0$   
 the charge flow from connecting wire =  $16\mu\text{C}$

**Ans 16**

(b)  $U_1 = \frac{1}{2} C_1 V^2 = \frac{1}{2} \times 2 \times (4)^2 = 16\mu\text{J}$

$U_2 = \frac{1}{2} C_2 V^2 = \frac{1}{2} \times 4 \times (4)^2 = 32\mu\text{J}$

Total energy stored =  $48\mu\text{J}$

**Ans 48**

(c)  $\Delta H = (U_i)_{\text{system}} - (U_f)_{\text{system}} = \frac{1}{2} \times 2 \times 12^2 - (16 + 32) = 96\mu\text{J}$

**Ans 96**

4. Charge after distribution

a  + 1/2nC  
 - 1/2nC

b  + 1/2nC  
 + 1/2nC

c  - 1/2nC  
 + 1/2nC

Charge on outer plate =  $\frac{\sum q}{2} = \frac{1}{2} \text{ nC}$ ;

$C = \frac{A \epsilon_0}{d} = \frac{500 \times 10^{-4} \times 8.85 \times 10^{-12}}{8.85 \times 10^{-3}} = 50 \text{ pF}$

charge on outer surface of upper plate is =  $\frac{1}{2} \text{ nC} = 0.5 \text{ nC}$  **Ans**

$V = \frac{q}{C} = \frac{0.5 \times 10^{-9}}{50 \times 10^{-12}} = 10 \text{ V}$  **Ans**

5. a  + 1/2nC  
 + 1/2nC charge on outer most plate =  $\frac{\sum q}{2} = \frac{1}{2} \text{ nC}$

b  - 1/2nC  
 + 1/2nC  $V_{ab} = \frac{q}{C} = \frac{1/2 \text{ nC}}{50 \text{ pF}} = 10 \text{ V}$  **Ans**

c  - 1/2nC  
 + 1/2nC  $V_{cd} = \frac{q}{C} = \frac{1/2 \text{ nC}}{50 \text{ pF}} = 10 \text{ V}$  **Ans**

6. When switch is open =  $C_{eq} = \frac{15}{2} \mu\text{F}$

$q_i = C_{eq} V = \frac{15}{2} \times 2 = 15 \mu\text{C}$

When switch is closed


$C_{eq} = 30 \mu\text{F}$

$q_f = 30 \times 2 = 60 \mu\text{C}$

Charge flow through AB =  $q_f - q_i = 45 \mu\text{C}$



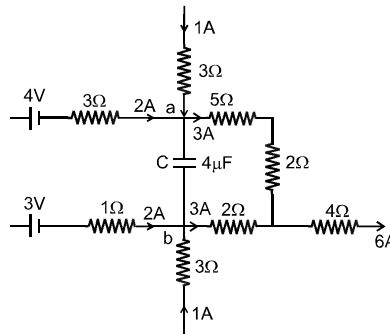7. Using Kirchoff's first law at junctions a and b, we have found the current in other wires of the circuit on which currents were not shown.



Now, to calculate the energy stored in the capacitor we will have to first find the potential difference  $V_{ab}$  across it.

$$V_a - 3 \times 5 - 3 \times 2 + 3 \times 2 = V_b$$


$$\therefore V_a - V_b = V_{ab} = 15 \text{ volt}$$

$$\therefore U = \frac{1}{2} CV_{ab}^2$$

$$= \frac{1}{2} (0.4 \times 10^{-6}) (15)^2 \text{ J} = 45 \mu\text{J}$$

**Ans.**


- 8.

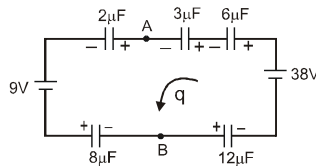

$$38 - \frac{q}{6} - \frac{q}{3} - \frac{q}{2} - 9 - \frac{q}{8} - \frac{q}{12} = 0 \quad \Rightarrow \quad q = 24 \mu\text{C}$$

$$V_A - \frac{24}{2} - 9 - \frac{24}{8} = V_B \quad V_A - V_B = 24 \text{ V} \quad \text{Ans}$$

9. at steady state

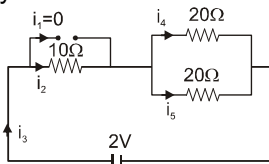

$$R_{eq} = 20\Omega \quad i_1 = 0 \quad \text{Ans}$$

$$i_3 = i_2 = \frac{2}{20} = \frac{1}{10} \text{ amp} \quad \text{Ans}$$

$$i_4 = i_5 = \frac{i_3}{2} = \frac{1}{20} \text{ amp} \quad \text{Ans}$$

$$\text{charge on capacitor } 6\mu\text{F is } = 6 \times 10^{-6} \times \frac{1}{10} \times 10 = 6\mu\text{C} \quad \text{Ans}$$

10. In steady state situation no current will flow through the capacitor,  $2\Omega$  and  $3\Omega$  are in parallel. Therefore, their combined resistance will be

$$R = \frac{2 \times 3}{2 + 3} = 1.2 \Omega$$

Net current through the battery :


$$i = \frac{60}{1.2 + 2.8} = 15 \text{ A}$$

This current will distribute in inverse ratio of their resistance  $2\Omega$  and  $3\Omega$ .

$$\therefore \frac{i_2}{i_3} = \frac{3}{2} \quad \text{or} \quad i_2 = \left( \frac{3}{3+2} \right) (15) = 9 \text{ A}$$



11.

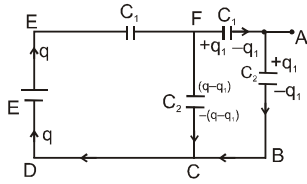

The distribution of charges is shown in figure In closed loop (CDEFC)

$$+E - \frac{q}{C_1} - \frac{(q - q_1)}{C_2} = 0 \quad \dots(i)$$

In closed loop (ABCFA)  $-\frac{q_1}{C_1} - \frac{q_1}{C_2} + \frac{q - q_1}{C_2} = 0$

or  $-\frac{q_1}{C_1} - \frac{q_1}{C_2} - \frac{q_1}{C_2} + \frac{q}{C_2} = 0$

or  $\frac{q}{C_2} = q_1 \left( \frac{2}{C_2} + \frac{1}{C_1} \right)$

or  $q = \left( \frac{2C_1 + C_2}{C_1} \right) q_1 \quad \dots(ii)$

From Eq.(i), we get  $E - \frac{q}{C_1} - \frac{q}{C_2} + \frac{q_1}{C_2} = 0$

or  $E + \frac{q_1}{C_2} = q \left( \frac{C_1 + C_2}{C_1 C_2} \right)$

or  $E + \frac{q_1}{C_2} = \left( \frac{2C_1 + C_2}{C_1} \right) q_1 \left( \frac{C_1 + C_2}{C_1 C_2} \right)$

or  $EC_2 + q_1 = \frac{(2C_1 + C_2)(C_1 + C_2)}{C_1^2} q_1$

or  $EC_2 = \frac{(2C_1^2 + 2C_1C_2 + C_1C_2 + C_2^2)}{C_1^2} q_1 - q_1$

$$EC_2 = \left\{ \frac{2C_1^2 + 3C_1C_2 + C_2^2 - C_1^2}{C_1^2} \right\} q_1$$


$\therefore q_1 = \frac{EC_2 C_1^2}{C_1^2 + 3C_1 C_2 + C_2^2}$

$$V_A - V_B = \left| \frac{-q_1}{C_2} \right| = \frac{q_1}{C_2}$$

$$= \frac{EC_1^2}{C_1^2 + 3C_1 C_2 + C_2^2} = \frac{E}{1 + 3\frac{C_2}{C_1} + \frac{C_2^2}{C_1^2}} = \frac{E}{1 + 3\eta + \eta^2} = 10V \left[ \because \frac{C_2}{C_1} = \eta = 2 \right]$$



12.

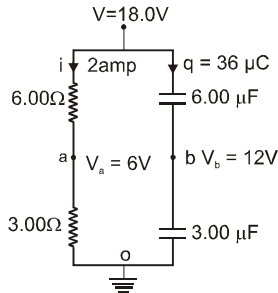

(i) When switch s is closed potential at b point is same as potential at a point

$$V_b = V_a = 6.0 \text{ Volt}$$


(ii) Final charge on  $6.0\mu\text{F}$  is  $q = 6 \times 12 = 72\mu\text{C}$  Therefore charge flow through wire b to a is

$$= 72 - 36 = 54 \mu\text{C}$$

13.

Let equivalent capacitance =  $C_{eq}$ .

Infinite ladder can be shown as :

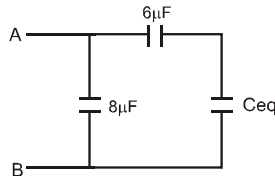

Now  $C_{eq}$  of this ladder,

$$C_{eq} = \frac{6}{6 + C_{eq}} + 8$$

by solving it,

$$C_{eq}^2 - 8 C_{eq} - 48 = 0$$


$$C_{eq} = 12 \mu\text{F} \quad \text{or} \quad -4 \mu\text{F}$$

neglecting -ve answer,

$$C_{eq} = 12 \mu\text{F}.$$

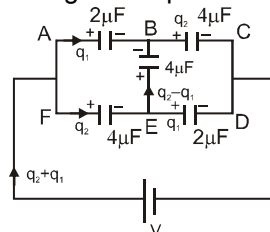14.

Charge on capacitor is assume as according to reverse symmetry.



$$q_1 + q_2 = C_{eq} V \quad \dots(i)$$

from loop AB EFA

$$-\frac{q_1}{2} + \frac{q_2 - q_1}{4} + \frac{q_2}{4} = 0 \Rightarrow 2q_2 - 3q_1 = 0 \quad \dots(ii)$$

from loop ABCA

$$-\frac{q_1}{2} - \frac{q_2}{4} + V = 0 \Rightarrow 4V = 2q_1 + q_2 \quad \dots(iii)$$

from (i), (ii) and (iii) we get

$$q_1 + \frac{3q_1}{2} = C_{eq} \left[ \frac{2q_1 + 3q_1}{4} \right] \Rightarrow C_{eq} = \frac{20}{7} \mu\text{F}$$

Ans




15.  $E = E_0 e^{-t/RC} \Rightarrow \frac{E_0}{3} = E_0 e^{-t/RC}$

$$\frac{1}{3} = e^{-4.4 \times 10^{-6} / R \times 2 \times 10^{-6}}$$

$$\ln 3 = \frac{11}{R5} \Rightarrow R = \frac{11}{5 \ln 3} = 2.0 \Omega.$$

16.

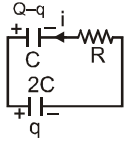

At time t using KVL  $\frac{Q-q}{C} - \frac{q}{2C} - iR = 0$

$$\frac{2Q-3q}{2C} - \frac{dq}{dt} R = 0 \Rightarrow \int_0^q \frac{dq}{2Q-3q} = \int_0^t \frac{dt}{2RC}$$

$$\frac{1}{-3} \ln \left( \frac{2Q-3q}{2Q} \right) = \frac{t}{2RC} \Rightarrow \frac{2Q-3q}{2Q} = e^{-\frac{3t}{2RC}} \Rightarrow q = \frac{2Q}{3} \left( 1 - e^{-\frac{3t}{2RC}} \right)$$

17. Let distance between the plates = d

$$18 \times 10^6 \times d = 4000$$

$$d = \frac{4000}{18 \times 10^6}$$

Now,  $C = \frac{\epsilon_r A \epsilon_0}{d}$

$$7.0 \times 10^{-2} \times 10^{-6} = \frac{10^{-9}}{36\pi} \times A \times 2.8 \times \frac{4000}{18 \times 10^6}$$

Solving, We get  $A = \frac{\pi}{5}$

18. Let a be the side of the square plate.

As shown in figure,  $C_1$  and  $C_2$  are in parallel. Therefore, total capacity of capacitors in the position shown is

$$C = C_1 + C_2$$

$$C = \frac{\epsilon_0 a(a-x)}{d} + \frac{K \epsilon_0 ax}{d}$$

$$\therefore q = CV = \frac{\epsilon_0 aV}{d} (a-x + Kx)$$

As plates are lowered in the oil, C increases hence charge stored will increase.

Therefore,  $i = \frac{dq}{dt} = \frac{\epsilon_0 aV}{d} (K-1) \cdot \frac{dx}{dt}$

Substituting the values

$$\epsilon_0 = 8 \times 10^{-12} \text{ C}^2/\text{N-m}^2$$

$a = 1\text{m}$ ,  $V = 500\text{ volt}$ ,  $d = 0.01\text{m}$ ,  $K = 11$  and  $\frac{dx}{dt} = \text{speed of plate} = 0.001\text{ m/s}$

We get current

$$i = \frac{(8 \times 10^{-12}) 1 (500) (11-1) (0.001)}{(0.01)} \text{ Amp.}$$


$$i = 4$$



**PART - III**

1. Electric field in the capacitor is same at every where which is equal to  $V/d$ . so that force at C and B point is same.  
 Electric field out side the capacitor is zero so that force at A point is zero.

2.

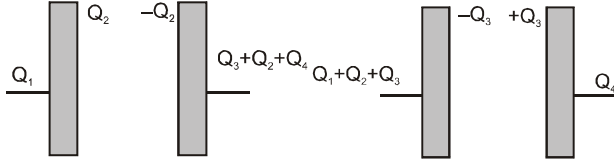

Charge on outer surfaces are equal so  $Q_1 = Q_3 + Q_2 + Q_4$  .....(i)  
 and  $Q_1 + Q_2 + Q_3 = Q_4$  .....(ii)

$$V = \left| \frac{Q_2}{C} \right| \text{ or } V = \left| \frac{Q_1 - Q_3 - Q_4}{C} \right|$$

$$V = \left| \frac{Q_3}{C} \right| \text{ or } V = \left| \frac{Q_1 - Q_2 - Q_4}{C} \right|$$

Adding (i) and (ii)

$$Q_1 = Q_4 \text{ and } Q_2 = -Q_3$$

3. (i)  $E_0 = \frac{2Q}{2\epsilon_0 A} - \frac{Q}{2\epsilon_0 A} = \frac{Q}{2\epsilon_0 A}$

$$E_{in} = \frac{2Q}{2A\epsilon_0} + \frac{Q}{2A\epsilon_0} \Rightarrow E_{in} = \frac{3Q}{2A\epsilon_0}$$

$$E_{in} = \frac{3Q}{2Cd} \Rightarrow E_{ind} = \frac{3Q}{2C} = V$$

(ii)  $F = EQ$

$$F = \left( \frac{2Q}{2A\epsilon_0} \right) \times (-Q) = -\frac{Q^2}{A\epsilon_0}$$

$$F = \frac{Q^2}{A\epsilon_0}$$

(iii) Energy =  $\frac{1}{2} \epsilon_0 E^2 Ad = \frac{1}{2} \epsilon_0 \left( \frac{3Q}{2Cd} \right)^2 A d = \frac{9}{8} \frac{Q^2}{C}$

4. equivalent capacitance before switch closed is  $C_{eq} = \frac{2C}{3}$ ,

Total charge flow through the cell is  $q = \frac{2CE}{3}$

equivalent capacitance after switch S closed is  $C_{eq} = 2C$


Total charge flow through the cell is  $q = 2CE$

Therefore some positive charge flow through the cell after closing the switch is  $= q_f - q_i = 2CE - \frac{2CE}{3} = \frac{4CE}{3}$

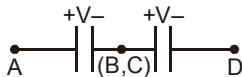5. the potential difference between end points may becomes zero.  
 the potential difference between end points may becomes 2V.




When terminal B is connected with terminal C



$$V_A - V_D = 2V$$



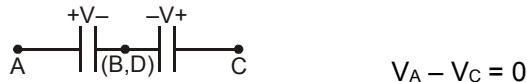When terminal B is connected with terminal D



$$V_A - V_C = 0$$

The energy stored in the system remains same.

$$6. \quad \frac{1}{C_{eq}} = \frac{1}{20} + \frac{1}{30} + \frac{1}{15} = \frac{3+2+4}{60}$$

$$C_{eq} = \frac{60}{9} = \frac{20}{3} \mu F$$

Total charge in this series combination is =  $\frac{20}{3} \times 90$

$$q = 600 \mu C$$

Potential difference between the plate of  $C_1$  is =  $\frac{q}{C_1} = \frac{600}{20} = 30V$


Potential difference between the plate of  $C_2$  is =  $\frac{q}{C_2} = \frac{600}{30} = 20V$

Potential difference between the plate of  $C_3$  is =  $\frac{q}{C_3} = \frac{600}{15} = 40V$

$$\frac{1}{C_{eq}} = \frac{1}{20} + \frac{1}{30} + \frac{1}{15} = \frac{3+2+4}{60}$$

$$C_{eq} = \frac{60}{9} = \frac{20}{3} \mu F$$

7.

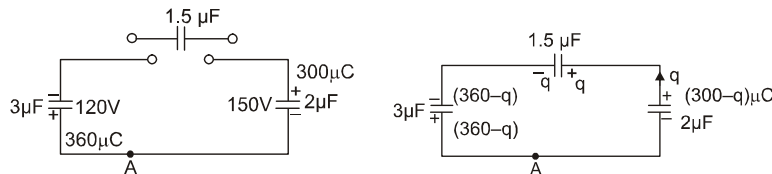

$$V_A + \frac{(300 - q)}{2} - \frac{q}{1.5} + \frac{360 - q}{3} = V_A \quad \dots\dots(i)$$

by solve this equation we get

$$\Rightarrow q = 180 \mu C$$

Charge on  $1.5 \mu F$  capacitor is =  $150 \mu C$

Charge on  $2 \mu F$  capacitor is =  $300 - 180 = 120 \mu C$

Therefore charge flows through A from left to right .

8. Magnitude of charge on the charged capacitor decreases and total charge is conserved.

At  $V_1 = V_2 \Rightarrow$  no further flow of charge occurs i.e. condition of steady state.

In charge flow energy is consumed in heat.

9.  $C = 2 \mu F$

$$C_{eq} = C + \frac{C}{2} + \frac{C}{4} + \frac{C}{8} + \frac{C}{16} + \dots$$

$$C_{eq} = C \left( \frac{1}{1 - 1/2} \right) = 2 \left( \frac{1}{1/2} \right) = 4 \mu F \quad \text{Ans}$$

Charge on first row capacitor is  $q_1 = 2 \times 10 \mu C = 20 \mu C$

Charge on second row capacitor is  $q_2 = 1 \times 10 \mu C = 10 \mu C$

Charge on third row capacitor is  $q_3 = 1/2 \times 10 \mu C = 5 \mu C$

Therefore charge on the capacitor in the first row is more than on any other capacitor.


Energy stored in all capacitor is =  $1/2 C_{eq} V^2 = 1/2 \times 4 \times 10^{-6} \times (10)^2 = 0.2 \text{ mJ}$  **Ans**

$C = 2 \mu F$





10.

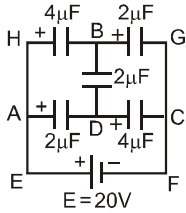

given  $V_C = 0$  in AEFC

$$V_A - 20 = V_C \Rightarrow V_A = 20 \text{ V} \quad \text{Ans}$$

by KCL, at point D

$$2(V_A - V_D) + 2(V_B - V_D) + 4(V_C - V_D) = 0$$

$$2(V_A - V_D) + 2(V_B - V_D) = 4V_D \quad \dots (i) \quad \text{Ans}$$

by KCL, at point B

$$4(V_A - V_B) + 2(V_D - V_B) + 2(V_C - V_B) = 0$$

$$4(V_A - V_B) + 2(V_B - V_D) = 2V_B \quad \dots (ii) \quad \text{Ans}$$

Adding eq (i) and (ii)

$$2(V_A - V_D) + 2(V_B - V_D) + 4(V_A - V_B) + 2(V_B - V_D) = 4V_D + 2V_B$$

$$\Rightarrow 6V_A = 6V_D + 6V_B$$

$$\Rightarrow V_A = V_D + V_B$$

11. In shown fig.  $C_2$  and  $C_3$  are parallel capacitor therefore  $V_2 = V_3$ .

Charge  $Q_1$  flow through battery and gone to  $C_1$  and divided into  $C_2$  and  $C_3$

$$Q_1 = Q_2 + Q_3,$$

$$\text{Total potential } V = V_1 + V_2 = V_1 + V_3 = V_1 + \frac{V_2 + V_3}{2}$$

12.  $q_{\max} = q_{01} = q_{02} =$  Both capacitors are charged up to the same magnitude of charge

$$t_2 > t_1$$

$$R_2 C_2 > R_1 C_1$$

$$q_{01} = C_1 V_1 = q_{02} = C_2 V_2$$

$$C_1 \neq C_2$$

So  $V_1 \neq V_2$ .

13.  $t_1 > t_2$

$$R_1 C_1 > R_2 C_2 \quad \text{for same } q_{\max}$$

$$q_{01} = q_{02} \Rightarrow E_1 C_1 = E_2 C_2$$


$$\text{If यदि } E_1 = E_2 \Rightarrow C_1 = C_2 \Rightarrow R_1 = R_2.$$

14. During decay of charge in RC circuit

$$I = I_0 e^{-t/RC}$$

$$\text{where } I_0 = \frac{q_0}{RC}$$
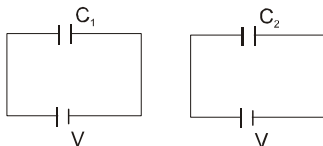
$$\text{when } t = 0, I = I_0 = \frac{q_0}{RC}$$



Since potential difference between the plates is same initially therefore  $I$  same in both the cases at  $t = 0$  and is equal to

$$I = \frac{q_0}{RC} = \frac{V}{R}$$



Also  $q = q_0 e^{-t/RC}$ . When  $q = \frac{q_0}{2}$  then  $\frac{q_0}{2} = q_0 e^{-t/RC}$

$\Rightarrow e^{+t/RC} = 2.$

$\frac{t}{RC} = \ln 2$


$\Rightarrow t = RC \log_e 2$

$\Rightarrow t \propto C$ . Therefore time taken for the first capacitor ( $1\mu\text{F}$ ) for discharging 50% of Initial charge will be less.

(B), (D) are the correct options.

15. A long time after closing the switch, system comes in steady state and no current flow through capacitor.

Circuit :

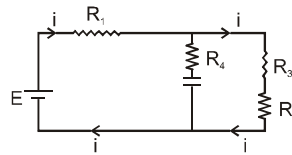

$i = \frac{E}{R_1 + R_2 + R_3}$

energy stored in battery =  $\frac{1}{2} CV^2 = \frac{1}{2} C \left( \frac{E (R_3 + R_2)}{R_1 + R_2 + R_3} \right)^2$

16.  $E = \frac{V}{d} \Rightarrow$  remains constant  
 $C' = KC \Rightarrow$  Increase  
 $Q' = KQ \Rightarrow$  Increase  
 $U = \frac{1}{2} KCV^2 = KU \Rightarrow$  Increase

17.  $C = \frac{\epsilon_0 A}{d}, C' = \frac{K \epsilon_0 A}{d} \quad Q = CV = \frac{\epsilon_0 KAV}{d} \quad \text{Ans}$

$Q = CV = C_1 V_1 \Rightarrow V_1 = \frac{V}{K} \quad E = \frac{V_1}{d} = \frac{V}{Kd} \quad \text{Ans}$

$W = U_f - U_i = \frac{1}{2} CV^2 - \frac{1}{2} C_1 V_1^2 = \frac{1}{2} \frac{\epsilon_0 AV^2}{d^2} - \frac{1}{2} \frac{K \epsilon_0 A}{d} \left( \frac{V}{K} \right)^2 = \frac{\epsilon_0 AV^2}{2d} \left( 1 - \frac{1}{K} \right) \quad \text{Ans}$

18. Battery connected  $V = \text{constant}$

$U' = \frac{1}{2} KCV^2 = KU \Rightarrow$  Increase by K-times

$E = \frac{V}{d} = \text{constant}$


$F = \frac{Q^2}{2 \epsilon_0 A} \Rightarrow F = \frac{C^2 V^2}{2 \epsilon_0 A} \Rightarrow F' = \frac{K^2 C^2 V^2}{2 \epsilon_0 A} = K^2 F$

$\Rightarrow$  Increase by  $K^2$ -times

$Q = CV \Rightarrow Q' = KCV = KQ \Rightarrow$  Increase by K-times.



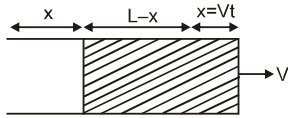19. Capacitance of capacitor is  $C_0 = \frac{k \epsilon_0 a L}{d}$



$$C = \frac{\epsilon_0 a x}{d} + \frac{k \epsilon_0 a (L-x)}{d}$$

$$C = \frac{a \epsilon_0}{d} [x + k(L-x)] = \frac{a \epsilon_0}{d} [kL - (k-1)x] = \frac{a \epsilon_0}{d} [kL - (k-1)vt]$$

So, C decreases linearly with time

Charge on capacitor  $Q = C_0 V_0 = \frac{k \epsilon_0 a L}{d} V_0 = \text{constant}$ .


Potential difference across plate is

$$V = \frac{Q}{C} = \frac{C_0 V_0}{C} \Rightarrow V \propto \frac{1}{C}$$

$$V = \frac{V_0}{\frac{a \epsilon_0}{d} [kL - (k-1)vt]}$$

Potential energy  $U = \frac{1}{2} QV = \frac{1}{2} C_0 V_0 V \Rightarrow U \propto V$  **Ans**

20.

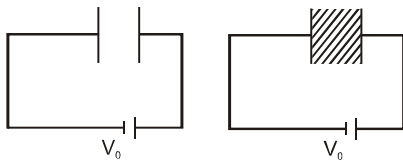

Potential difference =  $V_0$   
Capacitance =  $C$

$$Q_0 = CV_0$$

$$\text{Potential Energy} = \frac{1}{2} CV_0^2$$

Correct options are (A), (D).

Potential difference =  $V_0$   
Capacitance =  $KC$

[K is the dielectric constant of Slab  $K > 1$ ]  
New charge =  $KC V_0$

$$\text{New potential energy} = \frac{1}{2} KC V_0^2$$

21. In PQS process charge on capacitor is  $Q = CV$

In PSQ process charge on capacitor is  $Q' = KCV$

Electric energy stored in PQS is  $= \frac{1}{2} CV^2$

Electric energy stored in PSQ is  $= \frac{1}{2} KCV^2$

$$U_{PSQ} > U_{PQS}$$

Electric field in PS is  $E = \frac{V}{d}$

Electric field in SP is  $E = \frac{V}{d}$

$$E_{PS} = E_{SP}$$




**PART - IV**

**1 to 3.** When  $C_3 = \infty$ , there will be no charge on  $C_2$



As  $V_1 = 10\text{ V}$  therefore  $V = 10\text{ V}$

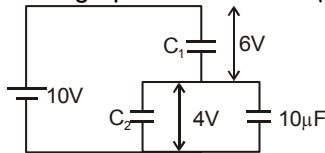From graph when  $C_3 = 10\ \mu\text{F}$ ,  $V_1 = 6\text{ V}$




Charge on  $C_1 = \text{Charge on } C_2 + \text{Charge on } C_3$

$$6C_1 = 4C_2 + 40\ \mu\text{C} \quad \dots (1)$$

Also when  $C_3 = 6\ \mu\text{F}$ ,  $V_1 = 5\text{ V}$

Again using charge equation

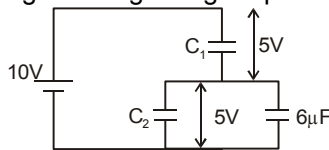

$$5C_1 = 5C_2 + 30\ \mu\text{C} \quad \dots(2)$$

Solving (1) and (2)

$$C_1 = 8\ \mu\text{F}, C_2 = 2\ \mu\text{F}.$$

**4 to 6.** For  $t = 0$  to  $t_0 = RC$  seconds, the circuit is of charging type. The charging equation for this time is


$$q = CE \left(1 - e^{-\frac{t}{RC}}\right)$$

Therefore the charge on capacitor at time  $t_0 = RC$  is  $q_0 = CE\left(1 - \frac{1}{e}\right)$

For  $t = RC$  to  $t = 2RC$  seconds, the circuit is of discharging type. The charge and current equation for this time are

$$q = q_0 e^{-\frac{t-t_0}{RC}} \quad \text{and} \quad i = \frac{q_0}{RC} e^{-\frac{t-t_0}{RC}}$$

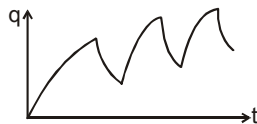Hence charge at  $t = 2RC$  and current at  $t = 1.5RC$  are



$$q = q_0 e^{-\frac{2RC-RC}{RC}} = \frac{q_0}{e} = \frac{1}{e} CE\left(1 - \frac{1}{e}\right)$$

$$\text{and} \quad i = \frac{q_0}{RC} e^{-\frac{1.5RC-RC}{RC}} = \frac{q_0}{\sqrt{e}RC} = \frac{E}{\sqrt{e}R} \left(1 - \frac{1}{e}\right) \text{ respectively}$$

Since the capacitor gets more charged up from  $t = 2RC$  to  $t = 3RC$  than in the interval  $t = 0$  to  $t = RC$ , the graph representing the charge variation is as shown in figure



### EXERCISE-3 PART - I

1. Equation of charging of capacitor,

$$V = V_0 \left( 1 - e^{-t/R_{eq}C_{eq}} \right)$$

$$C_{eq} = 2 + 2 = 4 \mu\text{F}$$

$$R_{eq} = 1 \text{ M}\Omega$$

$$4 = 10 \left( 1 - e^{-\frac{t}{10^6 \times 4 \times 10^{-6}}} \right)$$


$$e^{-t/4} = 0.6$$

$$\Rightarrow e^{t/4} = \frac{5}{3} \quad \Rightarrow \quad \frac{t}{4} = \ln 5 - \ln 3$$

$$\Rightarrow t = 0.5 \times 4$$

$$t = 2 \text{ sec.} \quad \text{Ans.}$$

- 2.

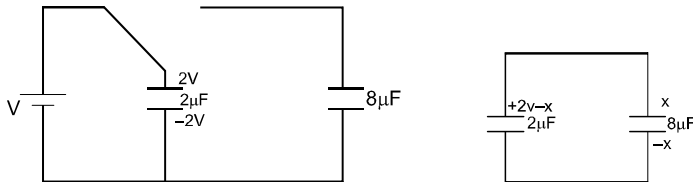

$$U_i = \frac{1}{2} (2)V^2, \quad V_{\text{common}} = \frac{V}{5}$$

$$U_f = \frac{1}{2} (2 + 8) \left( \frac{V}{5} \right)^2$$

$$\frac{U_i - U_f}{U_i} \times 100 = \frac{V^2 - \frac{V^2}{5}}{V^2} \times 100$$

$$\frac{4}{5} \times 100 = 80\% \text{ Ans.}$$

3.  $q_3 = \frac{C_3}{C_2 + C_3} \cdot Q$

$$q_3 = \frac{3}{3+2} \times 80 = \frac{3}{5} \times 80 = 48 \mu\text{C}$$

4. When switch  $S_1$  is released charge on  $C_1$  is  $2CV_0$  (on upper plate )  
 When switch  $S_2$  is pressed charge on  $C_1$  is  $CV_0$  (on upper plate ) and charge on  $C_2$  is  $CV_0$  (on upper plate)  
 When switch  $S_2$  is released and switch  $S_3$  pressed charge on  $C_1$  is  $CV_0$  (on upper plate ) and charge on  $C_2$  is  $-CV_0$  (on upper plate)

5.  $C = \frac{K\epsilon_0 A}{3d} + \frac{2\epsilon_0 A}{3d}$

$$C_1 = \frac{K\epsilon_0 A}{3d}$$

$$\frac{C}{C_1} = \frac{2+K}{K}$$

Ans. (D)



$$E_1 = E_2 = \frac{V}{d}$$



$$\Rightarrow \frac{E_1}{E_2} = 1 \quad \text{Ans. (A)}$$

$$Q_1 = C_1 V = \frac{K \epsilon_0 A}{3d} V$$

$$Q_2 = C_2 V = \frac{2 \epsilon_0 A}{3d} V$$

$$\Rightarrow \frac{Q_1}{Q_2} = \frac{K}{2}$$

6.

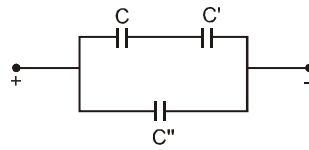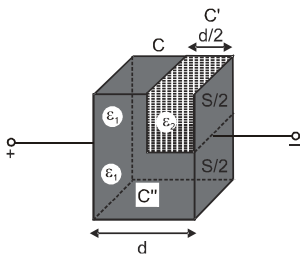


$$C_1 = \frac{\epsilon_0 A}{d}; \quad C = \frac{2 \epsilon_0 \frac{S}{2}}{\frac{d}{2}} = \frac{2 \epsilon_0 S}{d}$$

$$C' = \frac{4 \epsilon_0 \frac{S}{2}}{\frac{d}{2}} = \frac{4 \epsilon_0 S}{d}; \quad C'' = \frac{2 \epsilon_0 \frac{S}{2}}{d} = \frac{\epsilon_0 S}{d}$$

$$C_2 = \frac{C}{C+C'} + C'' = \frac{4 \epsilon_0 S}{3d} + \frac{\epsilon_0 S}{d} = \frac{7 \epsilon_0 S}{3d}$$

$$\frac{C_2}{C_1} = \frac{7}{3}$$

7.

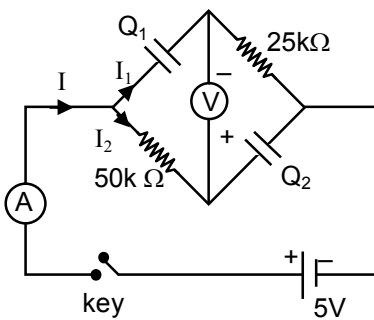

$$q_1 = (200 \times 10^{-3}) \left[ 1 - e^{-\frac{t}{\tau}} \right]$$

$$q_2 = (100 \times 10^{-3}) \left[ 1 - e^{-\frac{t}{\tau}} \right]$$



$$\frac{q_1}{C} = (50 \times 10^3) \frac{dq_2}{dt}$$

$$\frac{(200 \times 10^{-3})(1 - e^{-t})}{40 \times 10^{-6}} = (50 \times 10^3)(100 \times 10^{-3})[e^{-t}]$$

$$(1 - e^{-t}) \frac{10^6}{20} = 50 \times 10^3(e^{-t})$$

$$\frac{1}{2} = e^{-t}$$

$$t = \ln 2$$

$$I = I_1 + I_2 = (200 \times 10^{-3})(e^{-t}) + (100 \times 10^{-3})e^{-t}$$


$$= 100 \times 10^{-3}[2e^{-t} + e^{-t}]$$

$$= (300 \times 10^{-3}) e^{-t}$$

$$= \left( \frac{300 \times 10^{-3}}{e} \right)$$

At  $t = \infty$ ,  $I = 0$

8.

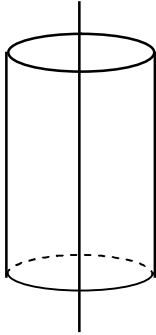

Suppose charge per unit length at any instant is  $\lambda$  and initially it is  $\lambda_0$   
 electric field at a distance  $r$  any instant is

$$E = \frac{\lambda}{2\pi\epsilon r}$$

$$J = \sigma \frac{\lambda}{2\pi\epsilon r}$$

$$\frac{dq}{dt} = J(A) = -J \times 2\pi r \ell$$

$$\frac{d\lambda \ell}{dt} = -\frac{\lambda}{2\pi\epsilon r} \times \sigma 2\pi r \ell$$

$$\lambda = \lambda_0 e^{-\frac{\sigma t}{\epsilon}}$$

$$J = J_0 e^{-\frac{\sigma t}{\epsilon}}$$

9.  $E_C = \frac{1}{2} CV_0^2$  ;  $E_D = V_0 CV_0 - \frac{1}{2} CV_0^2$

$$= \frac{1}{2} CV_0^2$$

$$\therefore E_C = E_D$$



$$10. \quad E_{D_1} = \frac{V_0}{3} \left( \frac{CV_0}{3} \right) - \frac{1}{2} C \left( \frac{V_0}{3} \right)^2 = \frac{CV_0^2}{9} - \frac{CV_0^2}{18}$$

$$= \frac{CV_0^2}{18}$$

$$E_{D_2} = \frac{2V_0}{3} \left[ \frac{2CV_0}{3} - \frac{CV_0}{3} \right] - \left[ \frac{1}{2} C \left( \frac{2V_0}{3} \right)^2 - \frac{1}{2} C \left( \frac{V_0}{3} \right)^2 \right]$$

$$= \frac{2V_0}{3} \left[ \frac{CV_0}{3} \right] - \frac{1}{2} C \left[ \frac{4V_0^2}{9} - \frac{V_0^2}{9} \right]$$

$$= \left( \frac{2}{9} - \frac{1}{2 \times 9} \times 3 \right) CV_0^2 = \left( \frac{2}{9} - \frac{1}{6} \right) CV_0^2 = \left( \frac{12-9}{9 \times 6} \right) CV_0^2$$

$$E_{D_2} = \frac{1}{18} CV_0^2$$

$$E_{D_3} = V_0 \left[ CV_0 - \frac{2CV_0}{3} \right] - \left[ \frac{1}{2} CV_0^2 - \frac{1}{2} C \left( \frac{2V_0}{3} \right)^2 \right]$$

$$= \frac{1}{3} CV_0^2 - \frac{1}{2} CV_0^2 \left[ 1 - \frac{4}{9} \right]$$



$$= \left( \frac{1}{3} - \frac{5}{18} \right) CV_0^2 = \left( \frac{6-5}{18} \right) CV_0^2 = \left( \frac{1}{18} \right) CV_0^2$$

$$\text{Total} = \left( \frac{1}{18} + \frac{1}{18} + \frac{1}{18} \right) CV_0^2$$

$$= \frac{3}{18} CV_0^2$$

$$E_D = \frac{3}{9} \left[ \frac{1}{2} CV_0^2 \right] = \frac{1}{3} \left( \frac{1}{2} CV_0^2 \right)$$

11.

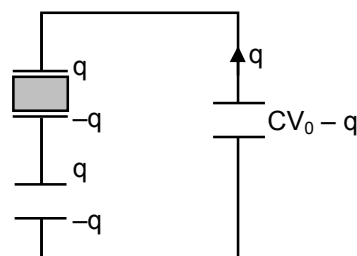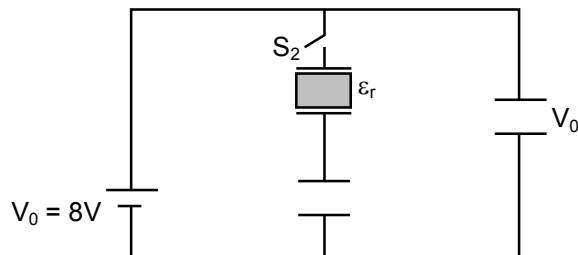

$$\frac{CV_0 - q}{C} - \frac{q}{\epsilon_r C} - \frac{q}{C} = 0$$

$$\frac{CV_0 - q}{C} = 5$$

$$5 = \frac{q}{C} \left( 1 + \frac{1}{\epsilon_r} \right)$$

$$8C - q = 5C$$






$$= 3 \left( 1 + \frac{1}{\epsilon_r} \right) \Rightarrow q = 3C$$


$$\frac{5}{3} = 1 + \frac{1}{\epsilon_r} \Rightarrow \frac{1}{\epsilon_r} = \frac{2}{3}$$

$$\epsilon_r = \frac{3}{2} = 1.5$$

12.

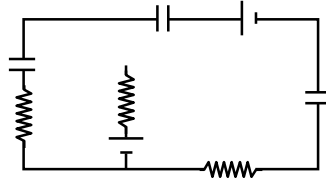


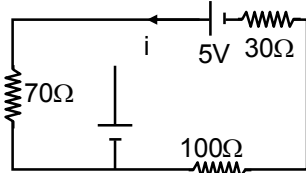Just after closing of switch  $S_1$  charge on capacitors is zero.  
 $\therefore$  Replace all capacitors with wire.



$$i = \frac{5}{70 + 100 + 30} = \frac{5}{200} = 25\text{mA}$$

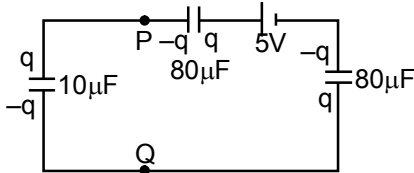Now  $S_1$  is kept closed for long time circuit is in steady state




$$\frac{q}{10} + \frac{q}{80} + \frac{q}{80} - 5 = 0$$

$$\frac{10q}{80} = 5$$

$$\therefore q = 40 \mu\text{C}$$

$$\therefore V \text{ across } C_1 = 40/10 = 4 \text{ volt}$$

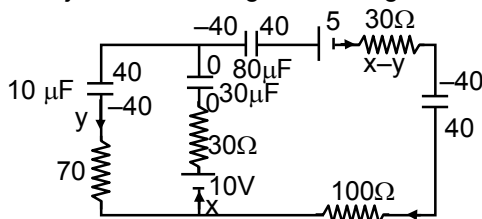Now just after closing of  $S_2$  charge on each capacitor remain same



KVL

$$-10 + x \times 30 + 40/10 + y \times 70 = 0$$

$$30x + 70y = 6 \quad \dots(1)$$

$$-\frac{40}{80} + 5 + (x - y) 30 - \frac{40}{80} + (x - y) \times 100 - 10 + x \times 30 = 0$$

$$160x - 130y - 6 = 0 \quad \dots(2)$$


$$y = 96/1510$$

$$x = 0.05 \text{ amp.}$$

**Correct option – 2, 3**



13.

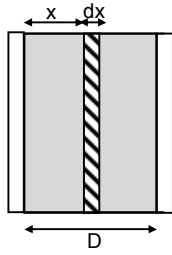

$$\frac{x}{m} = \frac{D}{N}$$

$$d\left(\frac{1}{C}\right) = \frac{dx}{K_m \epsilon_0 A} = \frac{dx}{K \epsilon_0 A \left(1 + \frac{m}{N}\right)} = \frac{dx}{K \epsilon_0 A \left(1 + \frac{x}{D}\right)}$$

$$\frac{1}{C_{eq}} = \int d\left(\frac{1}{C}\right) = \int_0^D \frac{D dx}{K \epsilon_0 A (D + x)}$$

$$\frac{1}{C_{eq}} = \frac{D}{K \epsilon_0 A} \ln 2$$

$$C_{eq} = \frac{K \epsilon_0 A}{D \ln 2}. \text{ Therefore } \alpha = 1$$

**PART - II**

1.  $U_0 = \frac{q_0^2}{2C} \quad U = \frac{q_0^2 e^{-2t_1/\tau}}{2C} = \frac{U_0}{2} = \frac{q_0^2}{4C} \quad \Rightarrow \quad e^{-2t_1/\tau} = \frac{1}{2}$

$$t_1 = \frac{\tau}{2} \ln 2 \quad \dots(1)$$


and  $q = q_0 e^{-t_2/\tau}$   
 $\frac{q_0}{4} = q_0 e^{-t_2/\tau},$

$$e^{-t_2/\tau} = \frac{1}{4}$$

$$t_2 = 2\tau \ln 2 \quad \dots(2)$$

$$\frac{t_1}{t_2} = \frac{1}{4}$$

2.

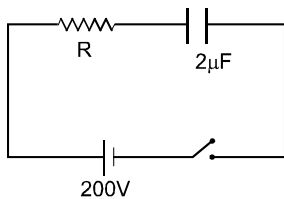

$$v = 200(1 - e^{-t/\tau})$$

$$120 = 200(1 - e^{-t/\tau})$$

$$e^{-t/\tau} = \frac{200 - 120}{200} = \frac{80}{200}$$

$$t/\tau = \log(2.5) = 0.4$$

$$5 = (0.4) \times R \times 2 \times 10^{-6}$$

$$\Rightarrow R = \frac{5}{(0.4) \times 2 \times 10^{-6}} = R = 2.7 \times 10^6$$

**Ans.**



3. Time constant for parallel combination =  $2RC$

Time constant for series combination =  $\frac{RC}{2}$

In first case :

$$V = V_0 e^{-\frac{t_1}{2RC}} = \frac{V_0}{2} \quad \dots\dots(i)$$

In second case :

$$V = V_0 e^{-\frac{t_2}{(RC/2)}} = \frac{V_0}{2} \quad \dots\dots(ii)$$

From (i) & (ii),

$$\frac{t_1}{2RC} = \frac{t_2}{(RC/2)} \Rightarrow t_2 = \frac{t_1}{4} = \frac{10}{4} = 2.5 \text{ sec.}$$

4.  $Q = C\epsilon_0 e^{-t/cR}$

$$4\epsilon = 4\epsilon_0 e^{-t/\tau}$$

$$\epsilon = \epsilon_0 e^{-t/\tau}$$

When  $t = 0 \Rightarrow \epsilon_0 = 25$

$$\epsilon = \epsilon_0 = 25$$

when  $t = 200 \Rightarrow \epsilon = 5$

$$5 = 25 e^{-\frac{200}{\tau}}$$

$$\ln 5 = \frac{200}{\tau}$$

$$\tau = \frac{200}{\ln 5} = \frac{200}{\ln 10 - \ln 2}$$

$$= \frac{200}{\ln 10 - 0.693}$$


**Alternative :**

Time constant is the time in which 63% discharging is completed.

So remaining charge =  $0.37 \times 25 = 9.25 \text{ V}$

Which time in  $100 < t < 150 \text{ sec.}$

5.

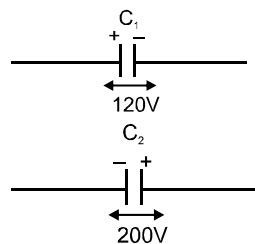

For potential to be made zero, after connection

$$120C_1 = 200 C_2$$

$$\Rightarrow 3C_1 = 5C_2$$


**Ans. (2)**

6. Electric field inside dielectric  $\frac{\sigma}{K\epsilon_0} = 3 \times 10^4$

$$\Rightarrow \sigma = 2.2 \times 8.85 \times 10^{-12} \times 3 \times 10^4 = 6 \times 10^{-7} \text{ C/m}^2$$





7.

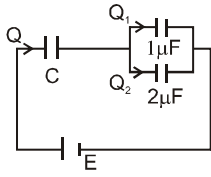


$$Q_2 = \frac{2}{2+1} \quad Q = \frac{2Q}{3}$$
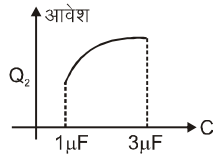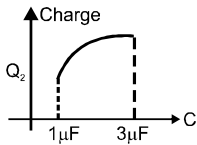
$$Q = E \left( \frac{C \times 3}{C+3} \right) \Rightarrow Q_2 = \frac{2}{3} \left( \frac{3CE}{C+3} \right) = \frac{2CE}{C+3}$$



8.

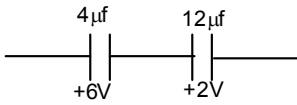

$$Q_1 = 24 \mu\text{C}$$


$$Q_2 = 18 \mu\text{C}$$

$$Q = 42 \mu\text{C}$$

$$E = 10^7 \times 42 \times 10^{-6}$$

$$E = 420 \text{ N/C}$$


9.

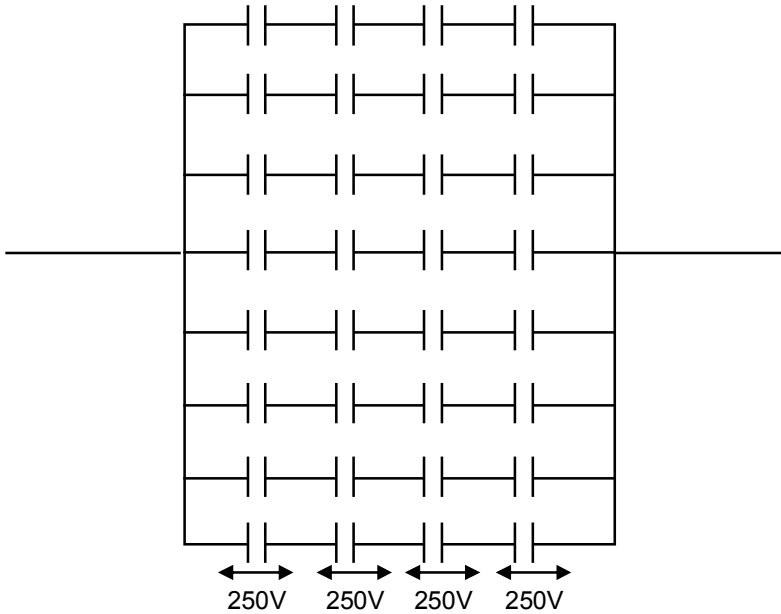


Minimum no. of capacitors required = 32



10.

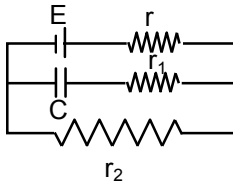

at steady state

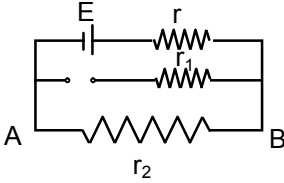

$$\text{current in the circuit } I = \frac{E}{r + r_2}$$

$$\text{potential difference across AB} = I r_2 = \frac{E r_2}{r + r_2}$$

$$\text{charge on capacitor} = Q = C(\Delta V)_{AB}$$


$$Q = \frac{C E r_2}{r + r_2}$$

11.  $Q_{\text{cap}} = K C_0 V$

$$|Q_{\text{polarised}}| = \left| Q_{\text{cap}} \left( 1 - \frac{1}{k} \right) \right|$$


$$= (90 \times 10^{-12}) (20) \left( \frac{5}{3} \right) \left( 1 - \frac{3}{5} \right) \text{ Coulomb} = 1200 \times 10^{-12} \text{ Coulomb} = 1.2 \text{ nc}$$

12.

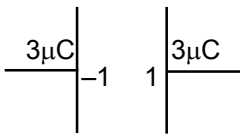

$$V = \frac{Q}{C} = \frac{1 \mu\text{C}}{1 \mu\text{F}} = 1 \text{ Volt}$$

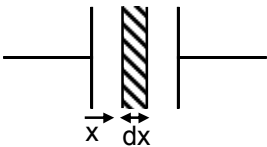13. Capacitance of element =  $\frac{k \epsilon_0 A}{dx}$



$$\text{Capacitance of element, } C' = \frac{K(1 + \alpha x) \epsilon_0 A}{dx}$$

$$\sum \frac{1}{C'} = \int_0^d \frac{dx}{K \epsilon_0 A (1 + \alpha x)}$$

$$\frac{1}{C} = \frac{1}{K \epsilon_0 A \alpha} \ln(1 + \alpha d)$$

Given  $\alpha d \ll 1$




$$\frac{1}{C} = \frac{1}{K\epsilon_0 A \alpha} \left( \alpha d - \frac{\alpha^2 d^2}{2} \right)$$

$$\frac{1}{C} = \frac{d}{K\epsilon_0 A} \left( 1 - \frac{\alpha d}{2} \right)$$

$$C = \frac{K\epsilon_0 A}{d} \left( 1 + \frac{\alpha d}{2} \right)$$

14.

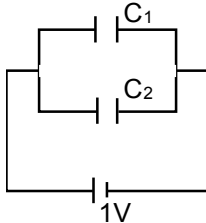

Given  $C_1 + C_2 = 10\mu\text{F}$  ... (i)

$$4 \left( \frac{1}{2} C_1 V^2 \right) = \frac{1}{2} C_2 V^2$$

$$\Rightarrow 4C_1 = C_2 \quad \dots \text{(ii)}$$

from equation (i) & (ii)

$$C_1 = 2\mu\text{F}$$

$$C_2 = 8\mu\text{F}$$


If they are in series

$$C_{\text{eq.}} = \frac{C_1 C_2}{C_1 + C_2} = 1.6\mu\text{F}$$




## SOLUTIONS OF HIGH LEVEL PROBLEMS

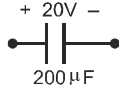1. (a) Charge on capacitor before connection



$$Q_1 = CV_1 = 4000 \mu\text{C}$$

Charge on capacitor after connection

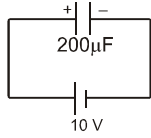

$$Q_2 = CV_2 = 200 \times 10 = 2000 \mu\text{C}$$

- (b) Charge flown through the 10V battery =  $4000 - 2000 = 2000 \mu\text{C}$

- (c) Work is done on the battery.

$$\text{Work done} = Q_2 \times V_2 = 2000 \times 10 = 20\text{mJ.}$$

- (d) The decrease in electrostatic field energy.

$$\begin{aligned} = U_i - U_f &= \frac{1}{2} CV_1^2 - \frac{1}{2} CV_2^2 = \frac{1}{2} \times 200 \times (20)^2 - \frac{1}{2} \times 200 (10)^2 \\ &= 30 \text{ mJ} \end{aligned}$$

- (e)  $W = \Delta U + \Delta H$

$$-20 \text{ mJ} = -30 \text{ mJ} + \Delta H$$

$$[\Delta H = 10 \text{ mJ}]$$

2. Equivalent capacitance =  $0.7 \mu\text{F} = \frac{7}{10} \mu\text{F}$


$$\frac{1}{C_{\text{eq}}} = \frac{1}{10} = \frac{1}{1 + \frac{3}{7}} = \frac{1}{1 + \frac{1}{7/3}} = \frac{1}{2 + \frac{1}{3}}$$

$C_{\text{eq}} = 0.7 \mu\text{F}$  can be obtain as shown in figure




$\frac{1}{3} \rightarrow$  Three capacitors in series

$2 \rightarrow$  2 capacitor in parallel.

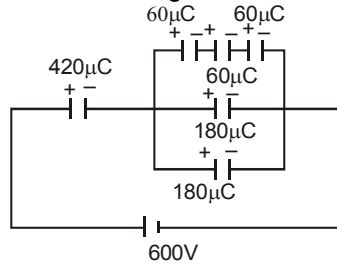and now charge distribute as shown in figure



3.  $Q = CV = 0.1 \times 10 = 1\text{C}$

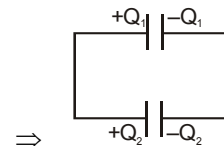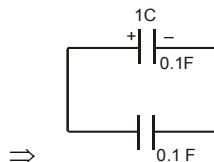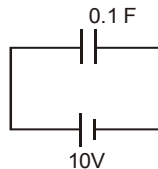

$$Q_2 = Q_1 = Q/2$$


$$U_{\text{initial}} = \frac{1}{2} \times 0.1 \times (10)^2 = 5 \text{ J}$$

$$U_{\text{final}} = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} \frac{Q^2}{C} = \frac{Q^2}{C}$$



$$= \left(\frac{1}{2}\right)^2 \times 10 = \frac{10}{4} = \frac{5}{2} \text{ J}$$
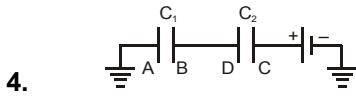
$$\frac{U_{\text{initial}}}{U_{\text{final}}} = \frac{5}{2.5} = 2$$




$$C_1 = \frac{\epsilon_0 \pi \left(\frac{0.1}{2}\right)^2}{2 \times 10^{-3}} = \frac{5\pi \epsilon_0}{4}$$

$$C_2 = \frac{\epsilon_0 \pi \left(\frac{0.12}{2}\right)^2}{3 \times 10^{-3}} = \frac{6\pi \epsilon_0}{5}$$

$$C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2} = \frac{30\pi \epsilon_0}{49} = \frac{30}{49 \times 36 \times 10^9} \approx 17 \text{ pF}$$

The energy stored  $U = \frac{1}{2} C_{\text{eq}} V^2$
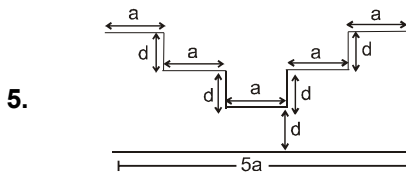
$$= \frac{1}{2} \times 17 \times (120)^2 \times 10^{-12} = 122.4 \text{ nJ}$$



This is combination of 5 capacitors connected parallel.

$$C = C_1 + C_2 + C_3 + C_4 + C_5 = \frac{(A/5)\epsilon_0}{d} + 2 \frac{(A/5)\epsilon_0}{2d} + 2 \frac{(A/5)\epsilon_0}{3d}$$

$$= \frac{A\epsilon_0}{5d} \frac{8}{3} = \frac{8\epsilon_0 A}{15d}$$

6. 
$$\frac{1}{dC} = \int \frac{dx}{K(x) \cdot A \epsilon_0} = \int_0^{d/2} \frac{dx}{\left[1 + \frac{\beta x}{\epsilon_0}\right] A \epsilon_0} + \int_{d/2}^d \frac{dx}{\left[1 + \frac{\beta x}{\epsilon_0}(d-x)\right] A \epsilon_0}$$

$$\int \frac{1}{dC} = \frac{1}{A \epsilon_0} \frac{\ell \ln \left[1 + \frac{\beta x}{\epsilon_0}\right]_0^{d/2}}{\frac{\beta}{\epsilon_0}} + \frac{1}{A \epsilon_0} \frac{\ell \ln \left[1 + \frac{\beta}{\epsilon_0}(d-x)\right]_d^{d/2}}{-\frac{\beta}{\epsilon_0}}$$

$$\int \frac{1}{dC} = \frac{1}{A\beta} \ell \ln \left[1 + \frac{\beta d}{2\epsilon_0}\right] + \frac{1}{A\beta} \ell \ln \left[1 + \frac{\beta d}{2\epsilon_0}\right]$$


$$C_{\text{eq}} = \frac{A\beta}{2\ell \ln \left[1 + \frac{\beta d}{2\epsilon_0}\right]}$$

Now  $C_{\text{eq}} = 2C_0$  ( $C_0$  = capacitance when it is without any dielectric)





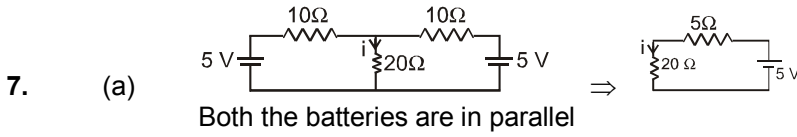
$$= \frac{A\beta}{2 \ln \left[ 1 + \frac{\beta d}{2 \epsilon_0} \right]} = \frac{2 \epsilon_0 A}{d} \quad \beta d = 4 \epsilon_0 \ln \left( 1 + \frac{\beta d}{2 \epsilon_0} \right)$$



Both the batteries are in parallel


$$i = \frac{5}{25} = \frac{1}{5} \text{ A}$$

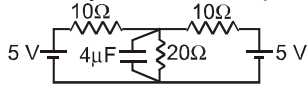(b) At steady state the capacitor will be fully charged.



Potential difference across capacitor  $v = \frac{1}{5} \times 20 = 4 \text{ V}$

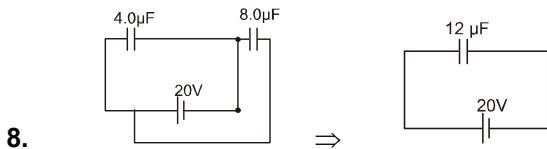
$$\text{Energy stored } U = \frac{1}{2} CV^2 = \frac{1}{2} \times 4 \times (4)^2 = 32 \mu\text{J}$$



(i) Charge flown through the battery  $Q = C_{eq} \cdot V = 240 \mu\text{C}$

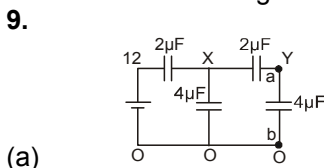(ii) Charge on  $4 \mu\text{F}$  capacitor  $= Q_{4\mu\text{F}} = 20 \times 4 = 80 \mu\text{C}$

Charge on  $8 \mu\text{F}$  capacitor  $= Q_{8\mu\text{F}} = 20 \times 8 = 160 \mu\text{C}$



By KCL,

$$(x - 12)2 + (x - 0) \cdot \frac{4}{3} + (x - 0) \cdot 4 = 0$$

$$2x - 24 + \frac{4x}{3} + 4x = 0$$

$$6x + \frac{4x}{3} = 24$$

$$x = \frac{36}{11} \text{ V}$$

$$(Y - 0) 4 = \left( \frac{36}{11} - Y \right) \times 2$$

$$(Y - 0) 2 = \left( \frac{36}{11} - Y \right)$$

$$2Y = \frac{36}{11} - Y$$


$$\left[ Y = \frac{12}{11} \text{ V} \right]$$

$$V_a - V_b = \frac{12}{11} \text{ V}$$

Ans.



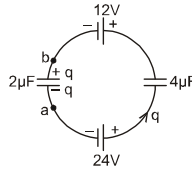(b)  $-12 - \frac{q}{2} + 24 - \frac{q}{4} = 0$



$$\frac{q}{2} + \frac{q}{4} = 12$$

$$\frac{3q}{4} = 12 \Rightarrow q = 16 \mu\text{C}$$

$$V_a - V_b = -\frac{q}{C} = -\frac{16}{2} = -8 \text{ V Ans.}$$

10. Before opening the switch potential difference across both the capacitors is  $V$ , as they are in parallel. Hence, energy stored in them is,

$$U_A = U_B = \frac{1}{2} CV^2 \quad \therefore U_{\text{Total}} = CV^2 = U_i \quad \dots\dots\dots (1)$$

After opening the switch, potential difference across it is  $V$  and its capacity is  $3C$

$$\therefore U_A = \frac{1}{2} (3C)V^2 = \frac{3}{2} CV^2$$

In case of capacitor B, charge stored in it is  $q = CV$  and its capacity is also  $3C$ . Therefore,


$$U_B = \frac{q^2}{2(3C)} = \frac{CV^2}{6}$$

$$\therefore U_{\text{Total}} = \frac{3CV^2}{2} + \frac{CV^2}{6} = \frac{10}{6} CV^2 = \frac{5CV^2}{3} = U_f \quad \dots\dots\dots (2)$$

From Eqs.(1) and (2)

$$\frac{U_i}{U_f} = \frac{3}{5}$$

- 11.

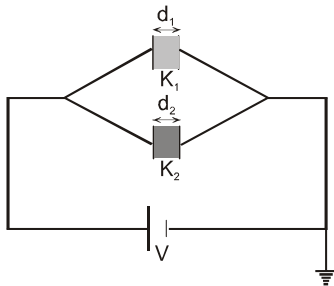


(a)  $C_{\text{eq}} = C_1 + C_2 = \frac{K_1 \epsilon_0 A}{d_1} + \frac{K_2 \epsilon_0 A}{d_2} = \epsilon_0 A \left( \frac{K_1}{d_1} + \frac{K_2}{d_2} \right)$

(b) Surface charge density =  $\frac{Q_1}{A} = \left( \frac{K_1 \epsilon_0 A}{d_1} \right) \frac{V}{A} = \frac{K_1 \epsilon_0}{d_1} V$  and  $\frac{Q_2}{A} = \left( \frac{K_2 \epsilon_0 A}{d_2} \right) \frac{V}{A} = \frac{K_2 \epsilon_0}{d_2} V$

(c) Energy density in medium  $K_1 = \frac{1}{2} K_1 \epsilon_0 E^2 = \frac{\epsilon_0 K_1 V^2}{2d_1^2}$



12.

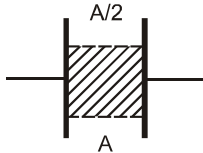

$$C_A = \frac{k \epsilon_0 A}{2d} + \frac{\epsilon_0 A}{2d}$$

$$(i) C_A = \frac{\epsilon_0 A}{2d} (k+1) = \frac{8.85 \times 10^{-12} \times 0.04}{2 \times 8.85 \times 10^{-4}} (9+1) = 2 \times 10^{-9} \text{ F} = 2 \text{ nF}$$

$$U_A = \frac{1}{2} C_A V^2 = \frac{1}{2} \times 2 \times 10^{-9} \times (110)^2 = 121 \times 10^{-7} \text{ J} = 12.1 \mu\text{J} \quad \text{Ans}$$

$$(ii) W = |U_f - U_i|$$

$$C_{\text{air}} = \frac{\epsilon_0 A}{d} = \frac{C_A \cdot 2}{k+1} = \frac{2 \times 10^{-9} \times 2}{10} = 0.4 \text{ nF} \quad Q = C_A V = 2 \times 10^{-9} \times 110 = 0.22 \mu\text{C}$$

$$U_f = \frac{1}{2} \frac{Q^2}{C_{\text{air}}} = \frac{1}{2} \frac{(0.22 \times 10^{-6})^2}{0.4 \times 10^{-9}} = 60.5 \mu\text{J}, \quad U_i = 12.1 \mu\text{J} \Rightarrow W = 48.4 \mu\text{J} \quad \text{Ans}$$


$$(iii) C_A = 0.4 \text{ nF}, Q_A = 0.22 \mu\text{C}, \quad C_B = \frac{k \epsilon_0 A}{d} = \frac{9 \times 8.85 \times 10^{-12} \times 0.02}{8.85 \times 10^{-4}} = 18 \times 10^{-10} \text{ F} = 1.8 \text{ nF}$$

$$\text{common potential } V = \frac{\text{total charge}}{\text{total capacitance}} = \frac{0.22 \times 10^{-6}}{(0.4 + 1.8) \times 10^{-9}} = 100 \text{ V}$$

$$U = \frac{1}{2} C_A V^2 + \frac{1}{2} C_B V^2 = \frac{1}{2} (C_A + C_B) V^2$$

$$= \frac{1}{2} (0.4 + 1.8) \times 10^{-9} (100)^2 = 11 \mu\text{J} \quad \text{Ans}$$

13. Equivalent circuit diagram

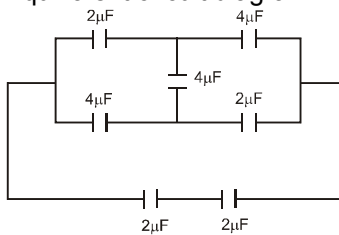


⇒ from part (a)



$$\text{Resultant capacitance} = \frac{20}{7} + 1 = \frac{27}{7} \mu\text{F}$$

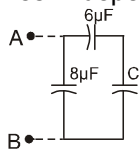14. If capacitance of C is equal to  $12 \mu\text{F}$ . Then equivalent capacitance of the ladder between points A and B is becomes independent of the number of section in between points.




$$\Rightarrow \frac{6C}{6+C} + 8 = C$$

$$\Rightarrow C^2 - 8C - 48 = 0 \quad \Rightarrow C = 12 \mu\text{F}$$



15.

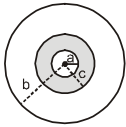

$$\int dV = \int E \cdot dr$$

$$V = \int_a^c \frac{q}{4\pi \epsilon_0 k r^2} dr + \int_c^b \frac{q}{4\pi \epsilon_0 r^2} dr = \frac{q}{4\pi \epsilon_0 k} \left[ -\frac{1}{r} \right]_a^c + \frac{q}{4\pi \epsilon_0} \left[ -\frac{1}{r} \right]_c^b$$

$$= \frac{q}{4\pi \epsilon_0} \left[ \frac{1}{k} \left( \frac{1}{a} - \frac{1}{c} \right) - \left( \frac{1}{c} - \frac{1}{b} \right) \right] = \frac{q}{4\pi \epsilon_0} \left[ \frac{bc - ab - kab + kac}{kabc} \right]$$

$$V = \frac{q}{4\pi \epsilon_0} \left[ \frac{ba(b-c) + b(c-a)}{kabc} \right]; C_{eq} = \frac{q}{V}$$


$$C_{eq} = \frac{4\pi \epsilon_0 kabc}{ka(b-c) + b(c-a)} = \frac{4\pi \epsilon_0 (3)(a)(3a)(2a)}{3a(3a-2a) + 3a(2a-a)}$$

$$C_{eq} = 3(4\pi \epsilon_0 a)$$

$$= 3(\text{capacitance of capacitor of isolated conducting shell of radius } a)$$

$$\Rightarrow n = 3$$

16.

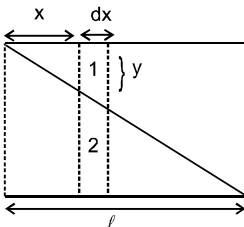

take 'dx' element at x distance  $\frac{x}{y} = \frac{l}{d}; y = \frac{x}{l} d$

$$dC_1 = \frac{K_2 b dx \epsilon_0}{y} = \frac{K_2 \epsilon_0 b dx}{x d}$$

$$dC_2 = \frac{K_1 b \epsilon_0 dx}{d-y} = \frac{K_1 b \epsilon_0 dx}{d(l-x)}$$

$dC_1$  and  $dC_2$  are in series, so their equivalent

$$dC = \frac{dC_1 dC_2}{dC_1 + dC_2} = \frac{K_1 K_2 b l \epsilon_0}{d} \frac{dx}{(K_1 - K_2)x + K_2 l}$$

Now, we can consider these parallel slabs to be parallel in circuit combination

$$C_{eq} = dC_1 + dC_2 + dC_3 + dC_4$$

$$= \int dC$$

$$= \int_0^l \frac{K_1 K_2 b l \epsilon_0}{d} \frac{dx}{(K_1 - K_2)x + K_2 l}$$

$$= \frac{K_1 K_2 b l \epsilon_0}{d(K_1 - K_2)} \{ \ln l K_1 - \ln K_2 l \}$$

$$C = \frac{K_1 K_2 b l \epsilon_0}{d(K_1 - K_2)} \ln \frac{K_1}{K_2} = \frac{K_1 K_2 b l \epsilon_0}{d(K_2 - K_1)} \ln \frac{K_2}{K_1}$$